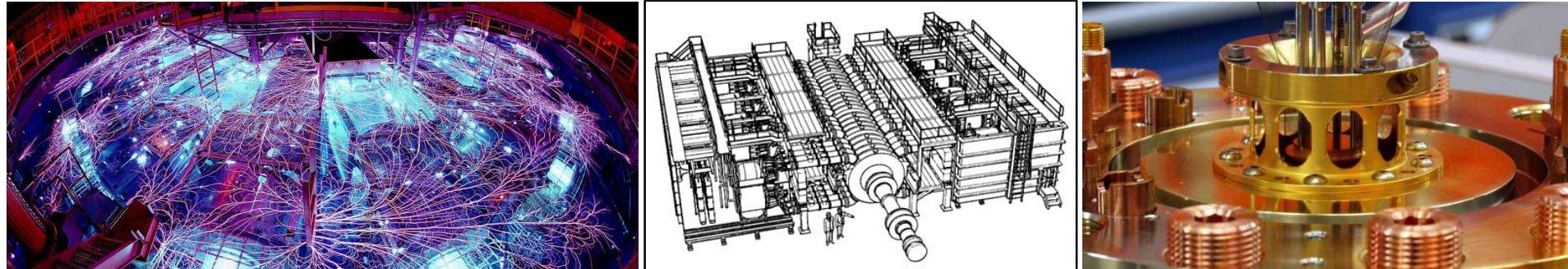


Exceptional service in the national interest



Pulsed Power: RLC Elements, Transmission Lines, and Marx Banks

Dr. William White

Z Pulsed Power Systems (01679)

20 January 2016



Sandia National Laboratories is a multi-program laboratory managed and operated by Sandia Corporation, a wholly owned subsidiary of Lockheed Martin Corporation, for the U.S. Department of Energy's National Nuclear Security Administration under contract DE-AC04-94AL85000. SAND NO. 2011-XXXX

Overview

- RLC Elements for Pulsed Power
- Transmission Lines for Pulsed Power
- Marx Banks
- Triggering of Marx Banks
- Applications of this Stuff!



Why Do Pulsed Power?

(Uhh... Besides Awesome Spaceship Battles?)

- Pulsed Power Squeezes Energy in Space and Time
- Lots of Applications Require “More”
 - Voltage
 - Current
 - Power

(All on Short Time Scales!)

- Examples...

X-ray Sources

High Energy Lasers

Microwave Sources

Fusion Experiments

Camera Flash Bulbs

High Energy Density Physics

Neutron Generators




Particle Accelerators
Electromagnetic Launchers
Laboratory Astrophysics

RLC Elements

- Resistors
 - Most Basic Element
 - Absorb Power
- Capacitors
 - Store Electrical Energy
- Inductors
 - Store Magnetic Energy
- Voltage and Current Sources Generate Energy
 - Batteries, Power Supplies
- Most Critical Elements for Pulsed Power (with Switches)




R

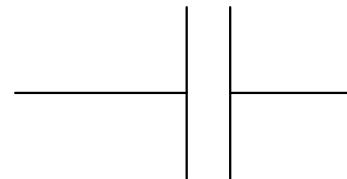

C


L

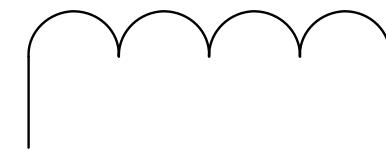

Ohm's Law and Power in Resistors

- How to Determine Current Flow in a Resistor:

$$V = I R$$

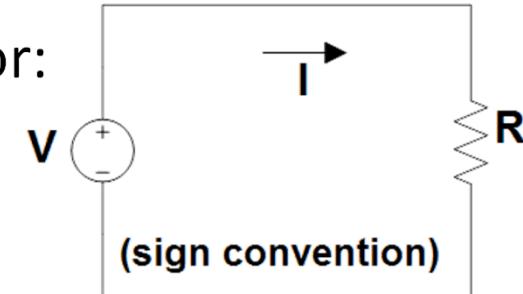

- Power Dissipated in a Resistor = Product of the Voltage and Current:

$$P = V I$$
$$P = I^2 \cdot R$$
$$P = \frac{V^2}{R}$$



Note that by Sign Convention, P is Always > 0
(Resistors Always Absorb Power)

Capacitors

- A capacitor = two conductors separated by an Insulator


- Capacitors Block DC
- Capacitors Store Electrical Energy
- Beware Voltage Reversals
- Generally Higher Power than Batteries
- Ideally Units have Pure Capacitance
 - Reality: Capacitors DO have Stray Inductances
 - Also Equivalent Series Resistance



Energy Storage in Capacitors


- Moving the Electric Charges onto the Plates Stores Energy

$$E_{cap} = \frac{1}{2} C \cdot V^2$$

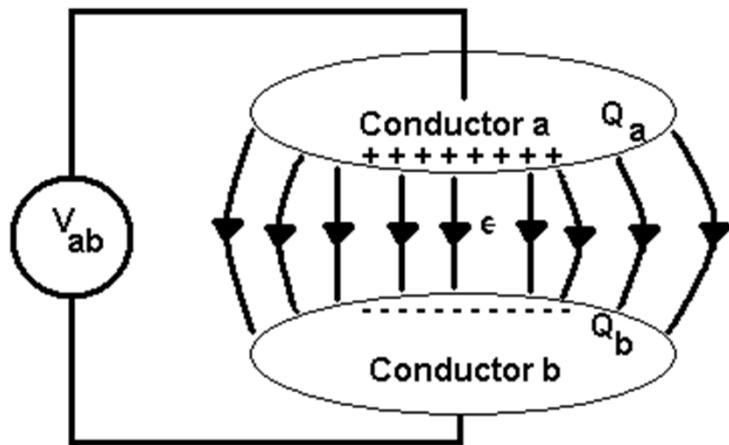


Inductors

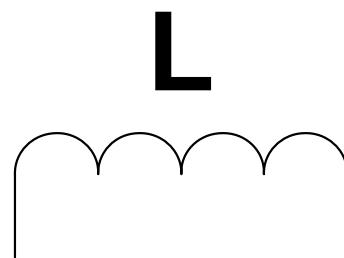- Current Flow in a Wire Loop Generates a Magnetic Field
 - To Change the Current, We Must Change the Magnetic Field Too...
 - A Voltage Develops: Inductance!



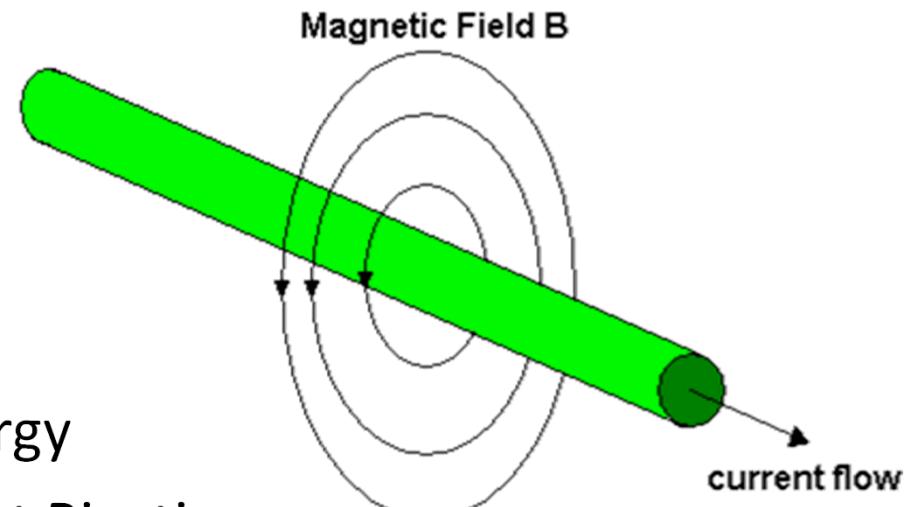- Inductors Block AC
- Inductors Store Magnetic Energy
- Load Inductance Limits Current Risetime




Energy Storage in Inductors

- Building up Current Stores Energy

- Analogously to Capacitors:
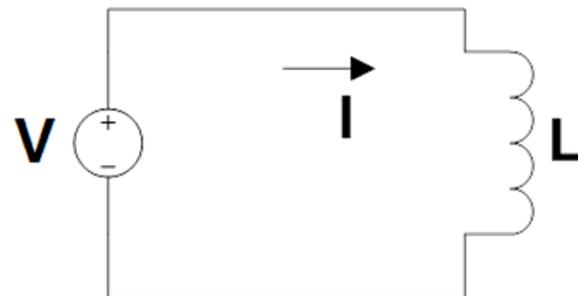
$$E_{\text{ind}} = \frac{1}{2} L \cdot I^2$$



Note: Inductors
have Stray
Capacitance Too!

Impedance of Inductors and Capacitors

- Use Laplace/Fourier Transforms to Make ~Ohm's Law:

$$v(t) = L \frac{di(t)}{dt} \Rightarrow \mathbf{F}\{v(t)\} \Rightarrow V = (j\omega \cdot L) \cdot I$$

$$i(t) = C \frac{dv(t)}{dt} \Rightarrow \mathbf{F}\{i(t)\} \Rightarrow V = \left(\frac{1}{j\omega \cdot C} \right) I$$

Impedance →
Each Term in the
Parentheses
Looks like a
Resistance
(with a Frequency
Dependence)

V = Voltage


I = Current

ω = radian frequency


$j = \sqrt{-1}$

These are Still
Lossless
Components

Transmission Lines

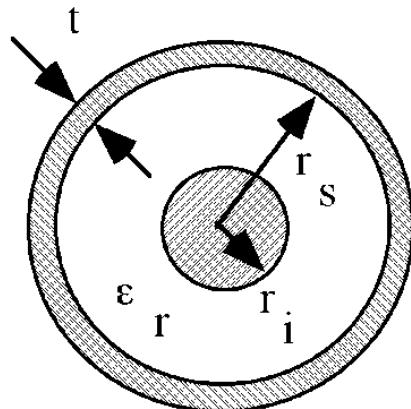


Coax

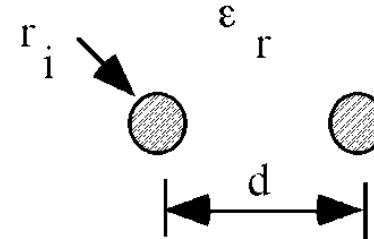


Parallel Conductors

(www.trantopcalc.sourceforge.net)

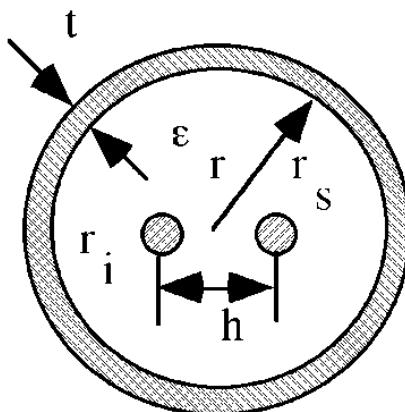


Balanced Shielded Line

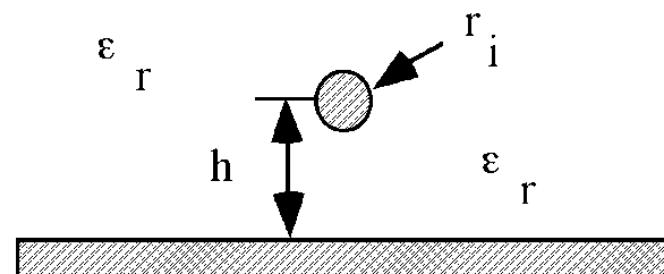

Single Wire Near Ground

Transmission Lines

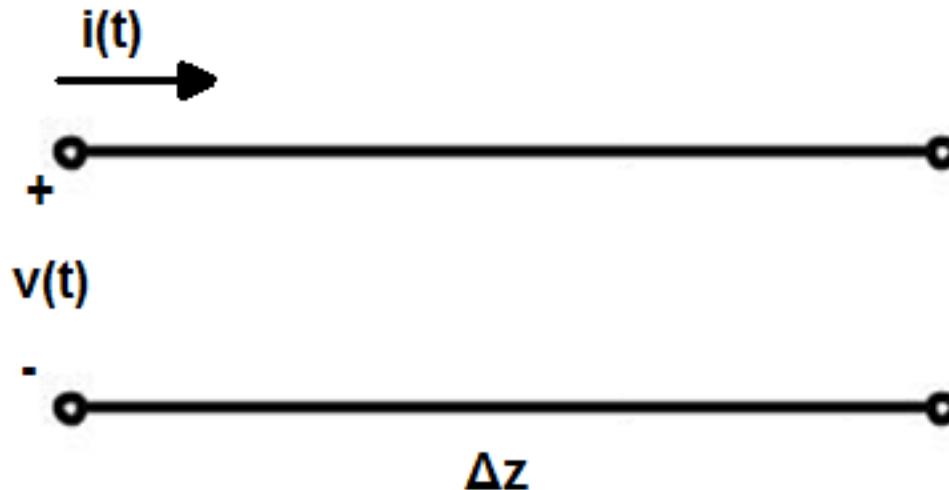- Voltage and Current are Defined at a Time (t) and Place (z)
- Solve for the Voltage/Current at One Location in Terms of Another;
 - Take the Limit as $\Delta z \rightarrow 0$



Solve for:

$$\frac{v(t)}{i(t)} = Z_o$$

Impedance!

(Note: Impedance Z_o is not the same as distance z along the transmission line)

Lossless Transmission Lines

- Make a Simplifying Assumption (no losses)
 - Solve for **Impedance** and **Phase Velocity**:

$$\therefore Z_o = \sqrt{\frac{R + j\omega L}{G + j\omega C}};$$

$$R, G = 0 \rightarrow$$

$$Z_o = \sqrt{\frac{L}{C}}$$

(Note: Impedance Z_o is not the same as distance z along the transmission line)

$$\therefore v_p = \frac{\omega}{\beta} = \frac{\partial z}{\partial t};$$


$$\beta \left(= \frac{2\pi}{\lambda} \right) = \omega \sqrt{LC} \rightarrow$$

$$v_p = \frac{1}{\sqrt{LC}}$$

Length of
Transmission
Line Sets
Pulsewidth!

Impedance Again?

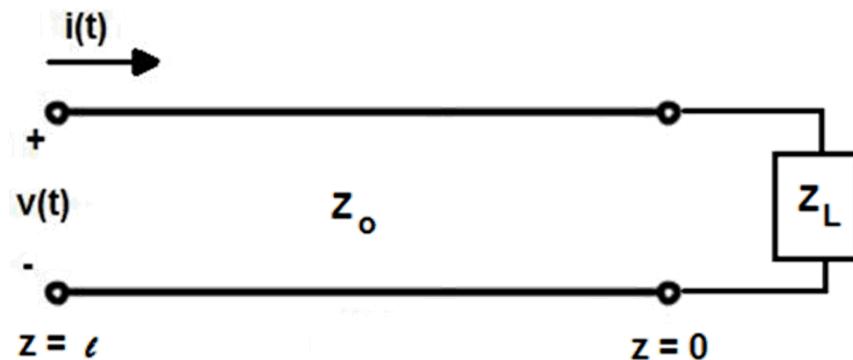- Impedance is a Characteristic of the EM Wave as Energy 'Flows' Down the Transmission Line
 - NOT a DC Resistance
 - Generally Dependent upon Frequency
- Changes in Impedance Generate Reflections
 - These are Required by the Boundary Conditions on the EM Wave
- Also Useful for Pulseshaping
- Matched Impedances → Maximum Power Flow



$Z_L \ll Z_o \Rightarrow$ Voltages cancel at the load

Negative reflected wave

$Z_L \gg Z_o \Rightarrow$ Currents cancel at the load,


Positive reflected wave

$Z_L = Z_o \Rightarrow$ No apparent transition

No reflected wave!

RLC's and Transmission Lines

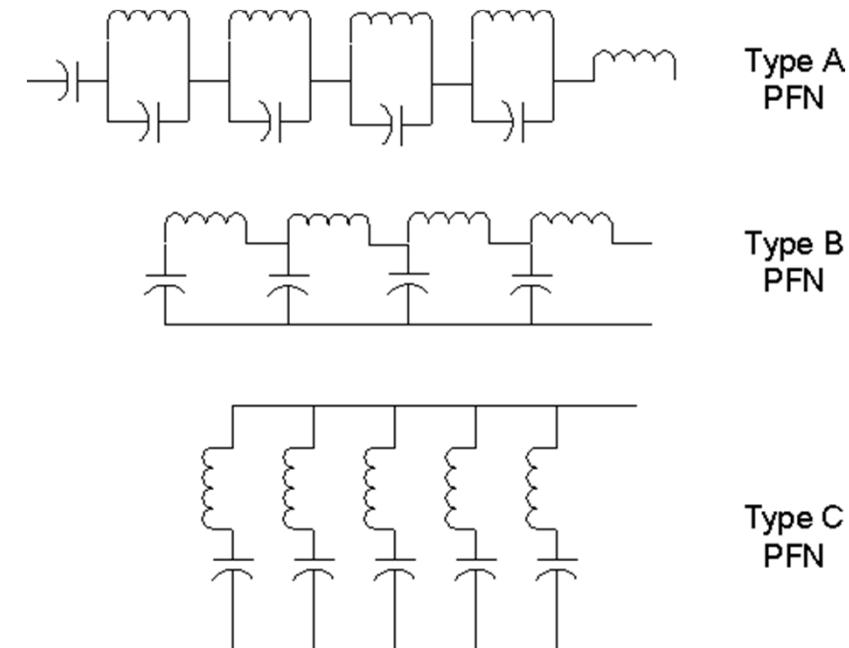- For Pulsed Power these Concepts are Complementary
 - TLines are analyzed using RLC components (per unit length)
 - We Construct TLines from Discrete Components
 - We Use TLines to Approximate Discrete Components
 - We use TLine Models to Simulate Discrete Components
- Detailed Applications Drive Which Topology is Selected




E.g.: Guillemin Equivalent Networks

Marx Banks



Marx Banks vs. Parallel Capacitor Banks


- Capacitor Banks Store Energy
- Marx Banks Store Energy AND Multiply the Voltage
- Marx Banks Charge Over Seconds, Discharge in Microseconds

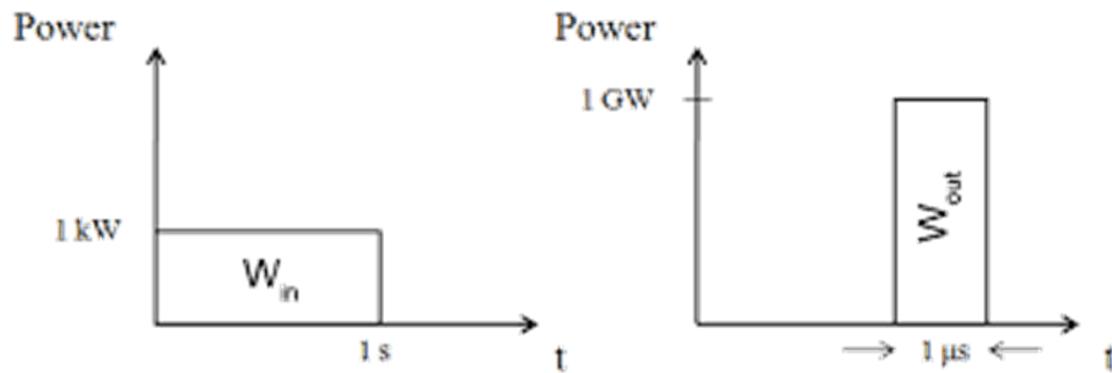

No 5.4 MV Duracell's (Yet!)


Basic Marx Bank

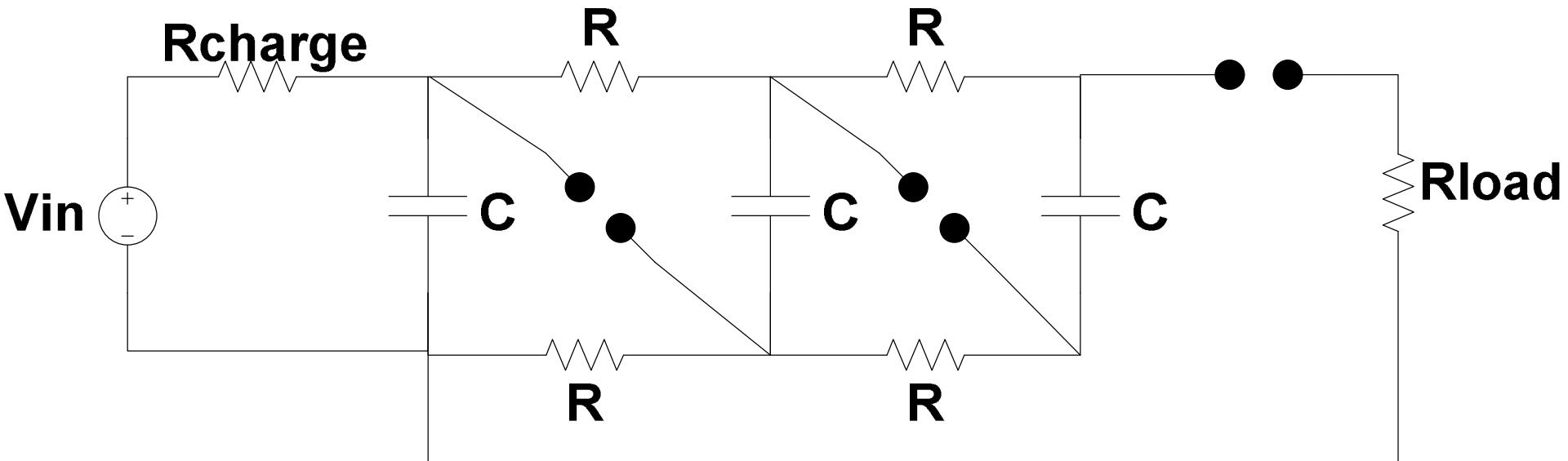- Fast Switches Allow Parallel Charging
 - Discharge in Series




- Commonly Use Spark Gap Switches, Ignitrons
 - Novel Solid State Switches are Appearing!

Basic Marx Bank Analysis: Charging

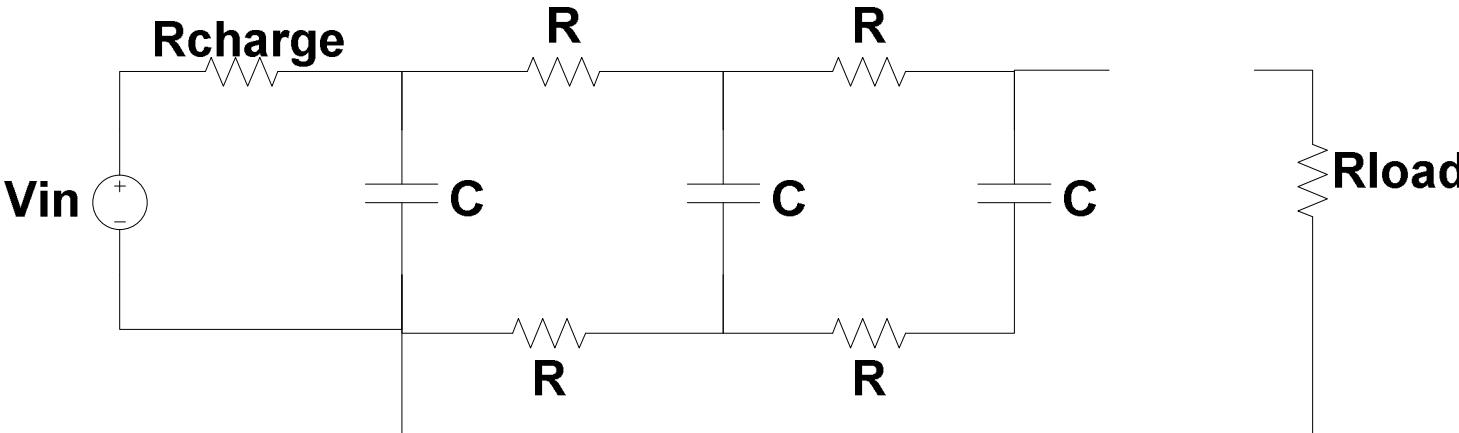


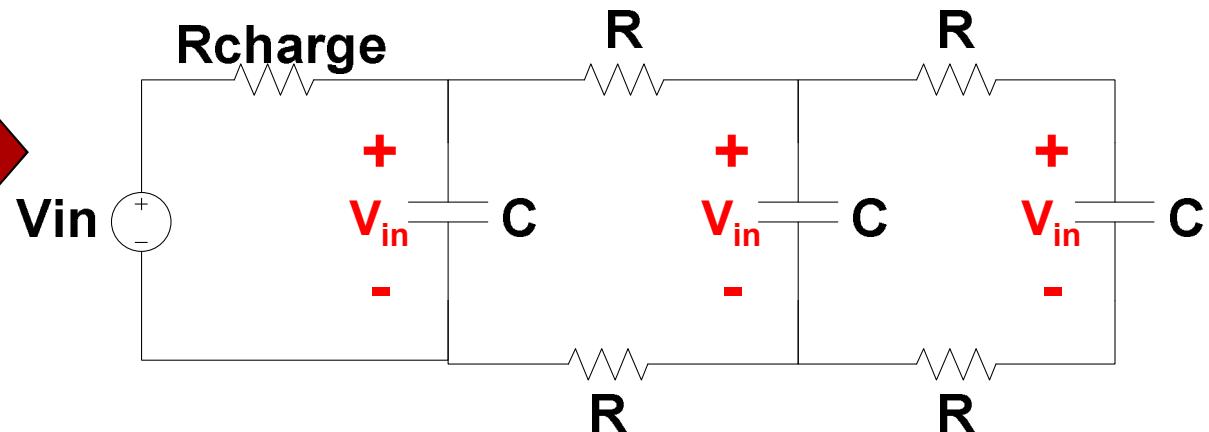Since No
Current Flows
Through R_{load} ,
the Circuit can
be Simplified




After “A Long Time”

Basic Marx Bank Analysis: Discharging

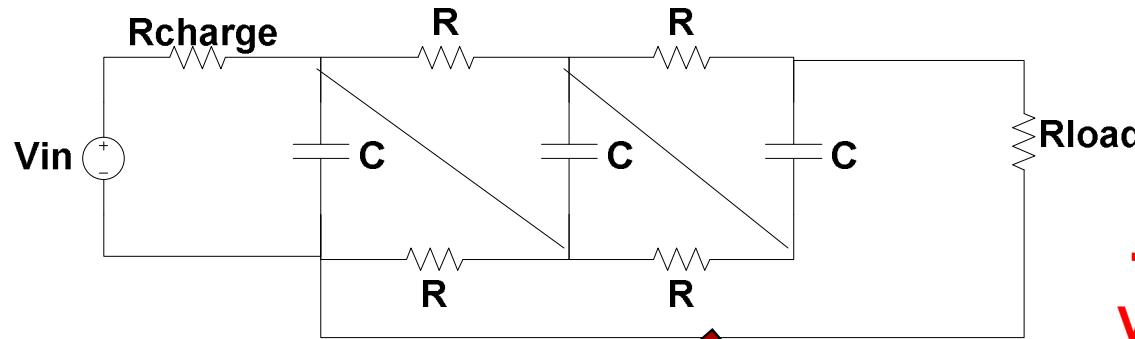


**Redraw the
Circuit:**

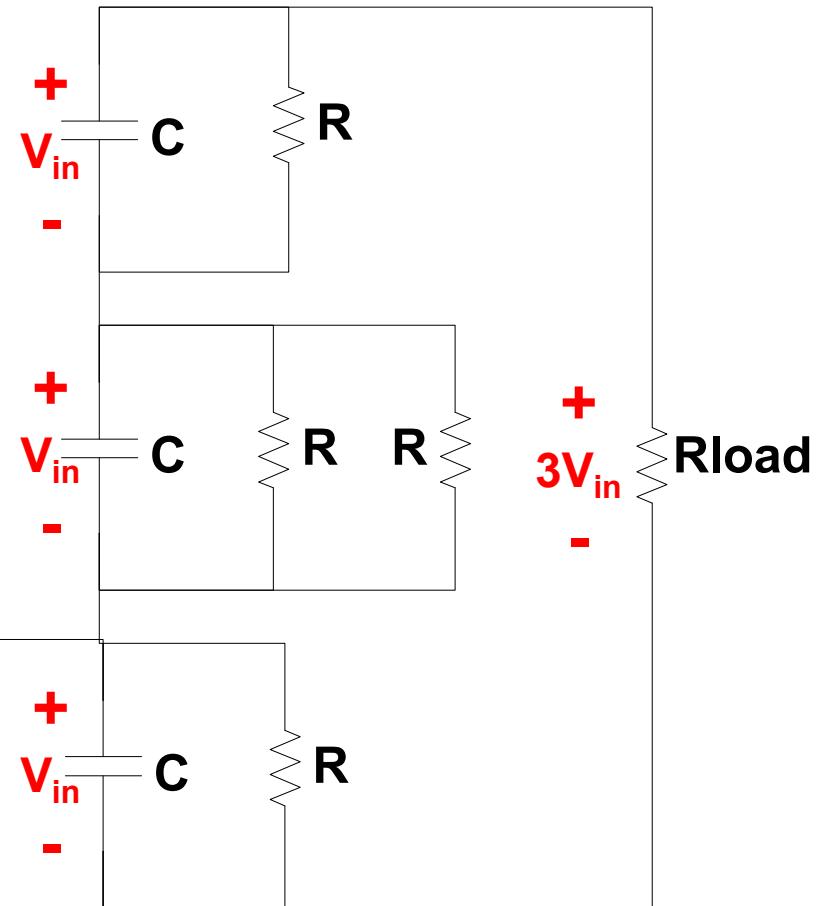**Output Voltage is
Multiplied by the
Number of
Stages!**




Bipolar Marx Bank:

Charging/Discharging

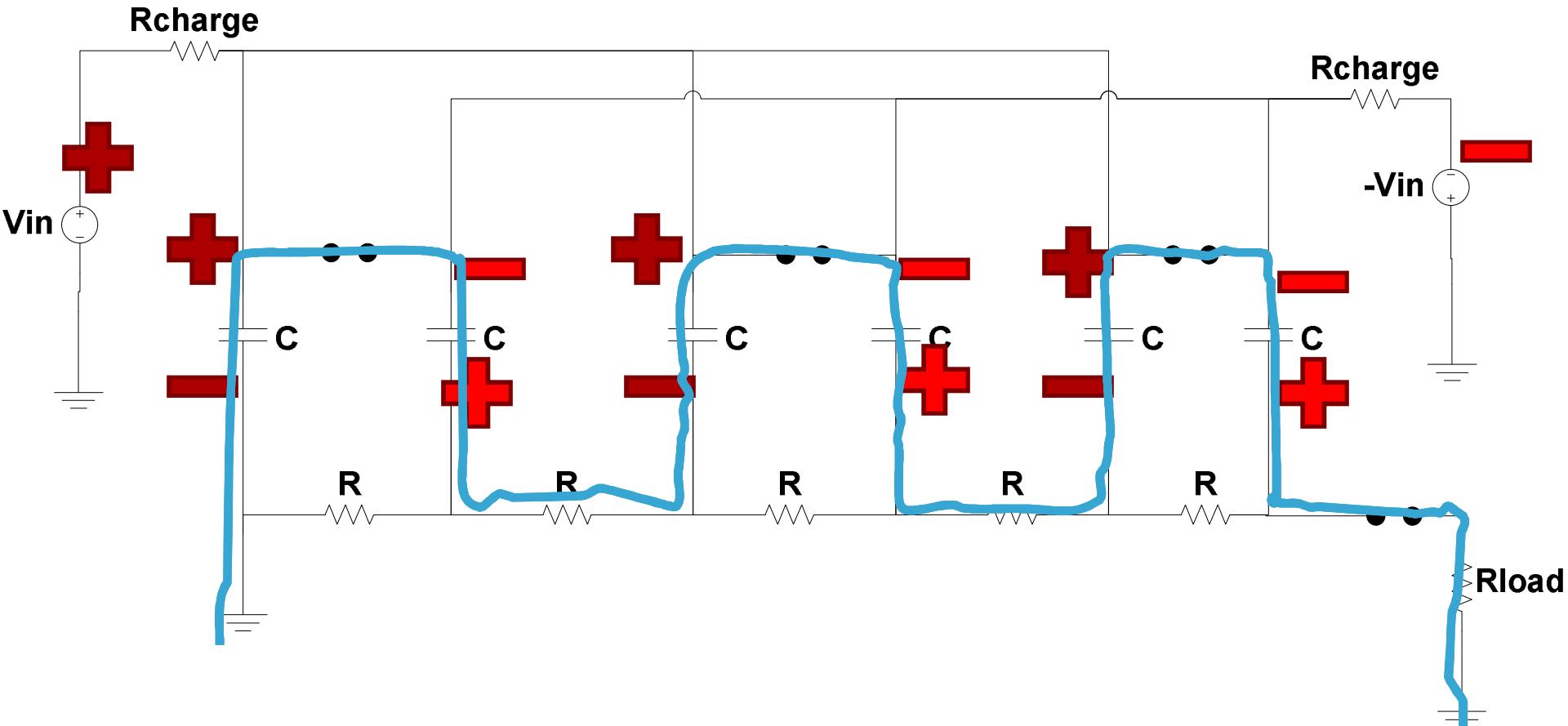


Z Main Marx Bank :

Charging/Discharging

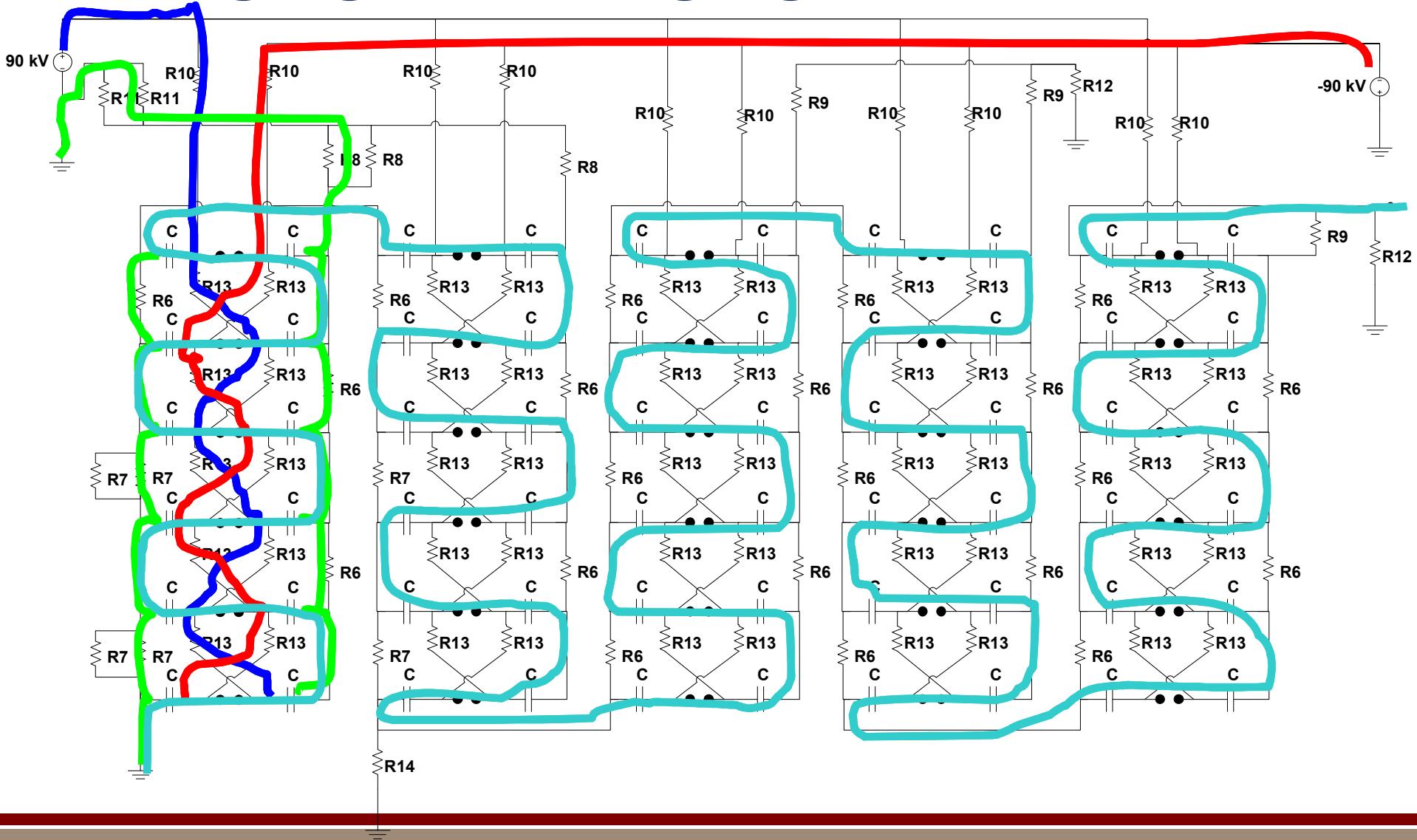


Triggering Marx Banks

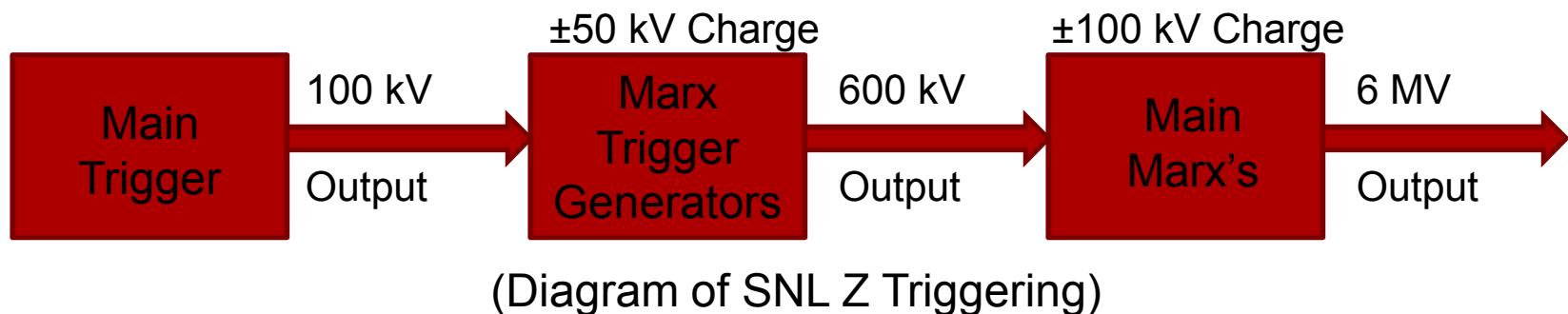
- Triggers are Usually Staged
- In Many Systems, Each Switch has Dedicated Triggers
- Other Marx Banks Only Supply Triggers to Early Stages
- Those Stages Trigger Later Sections
 - **Reduced Jitter!**



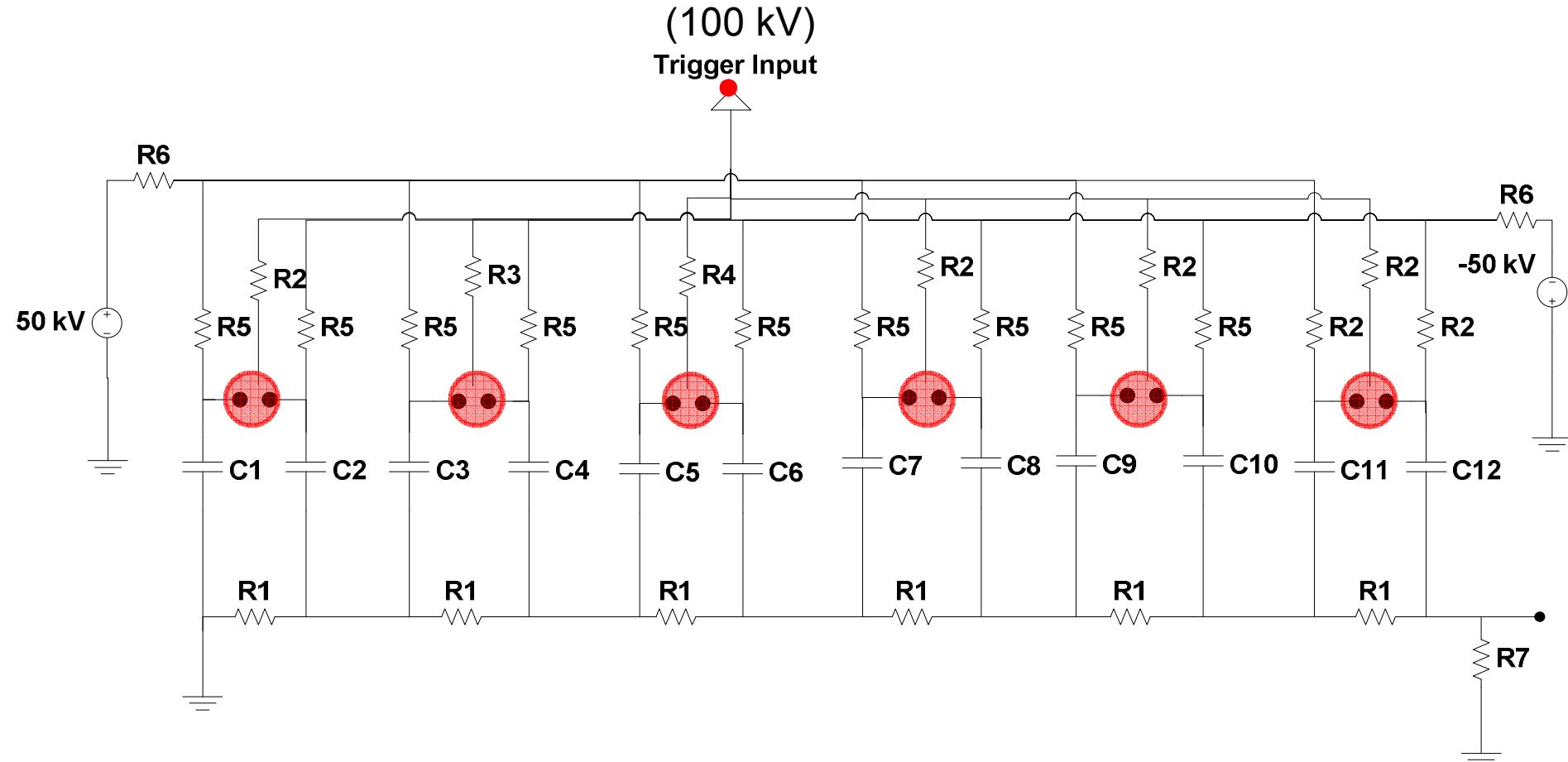Marx Triggering: All Switches Externally Triggered



Z Main Marx Triggering (First 3 Rows)

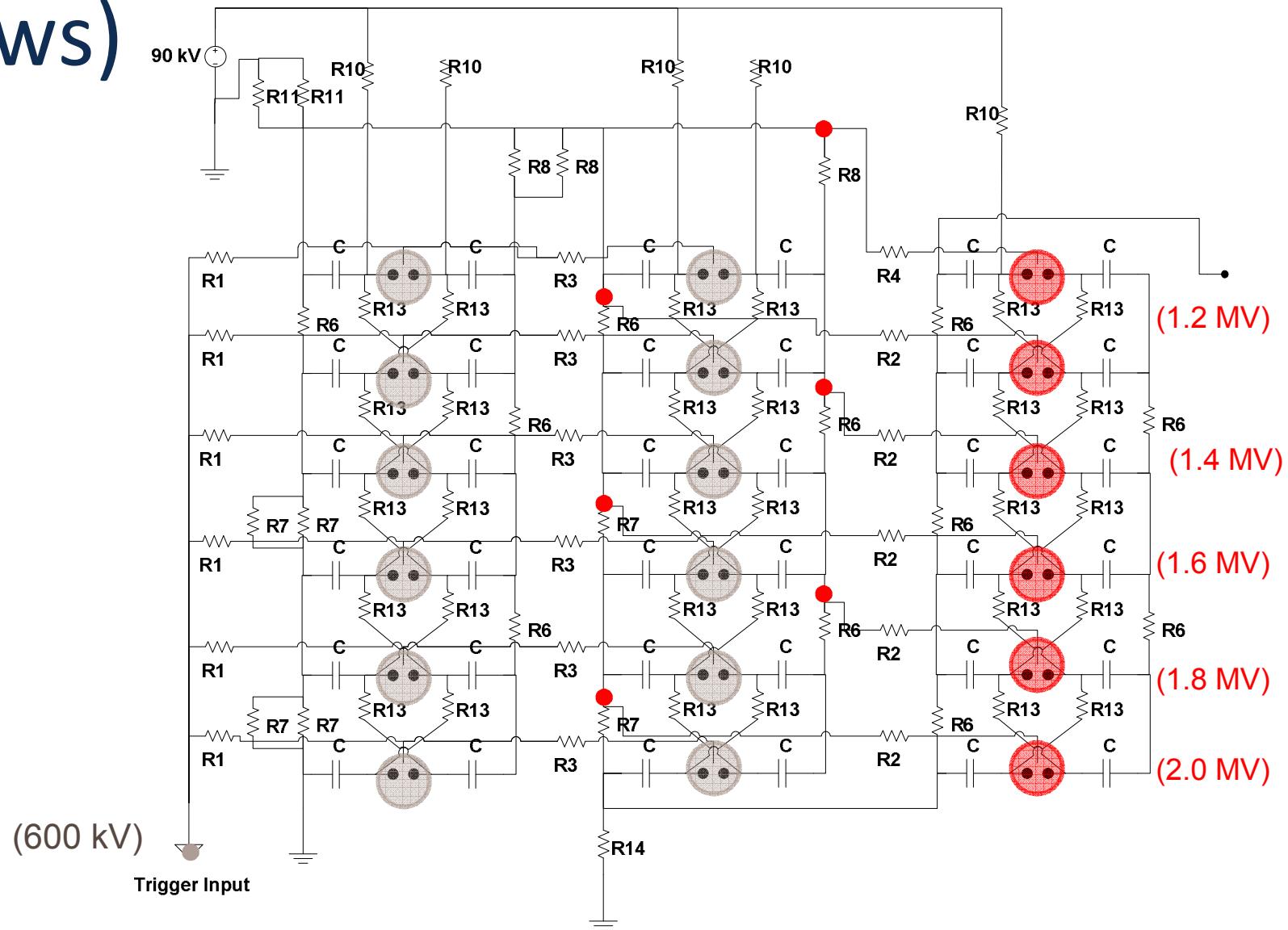

What Can We Do With All This?



Build AFRL's SHIVA Star



Or SNL's
Saturn



Or Various Iterations of SNL Z Machine:

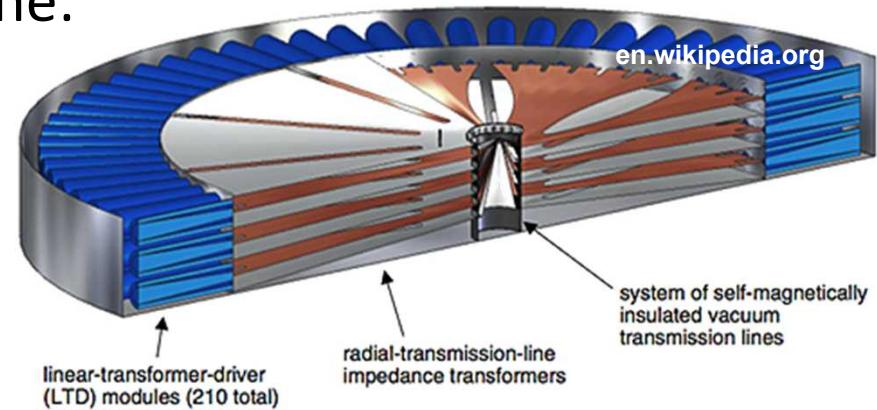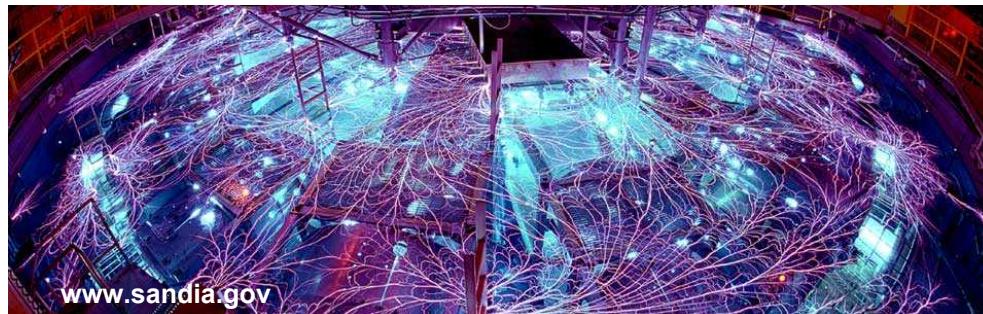

Summary

- Reviewed Basic Electrical Components for Pulsed Power
- Reviewed Transmission Lines for Pulsed Power
- Learned About Marx banks and How to Trigger Them
- Things we didn't mention: Inductive Energy Stores, Blumleins, Solid State Triggering, Metamaterials...

To Learn More...

- There are lots of good books on the subject:
 - *J.C. Martin on Pulsed Power*, by T.H. Martin, et al, 1996
 - *Pulsed Power*, by G.A. Mesyats, 2005
 - *Transient Electronics*, by P.W. Smith, 2002
 - *High Speed Pulse Technology (2 vols.)*, by F. Frungel, 1965
 - *Pulse Generators (MIT Rad Lab Series)*, by Glasoe and Lebacqz, 1948
 - *Electronic Gadgets for the Evil Genius*, by B. Iannini, 2004
- Try the Power Modulator/High Voltage conference this summer (San Francisco, CA):
<http://www.ipmhvc.com/2016/>
- Also Texas Tech has their annual short course:
<http://www.p3e.ttu.edu/shortcourse2015/>
- The Pulsed Power Formulary is available for free online:
http://www.highvoltageprobes.com/_literature_89707/Pulsed_Power_Formulary
- As is material from the US Particle Accelerator School (e.g.):
http://uspas.fnal.gov/materials/09VU/VU_PulsedPowerEng.shtml
- Finally, this guy builds smaller pulsed power stuff:
<http://www.electricstuff.co.uk/marxgen.htm>

Want to do Cool Stuff Like This?



Check out our website:
sandia.gov/careers

Sandia National Laboratories

Locations Contact Us Employee Locator Search

ABOUT PROGRAMS RESEARCH WORKING WITH SANDIA NEWS CAREERS

Students and Postdocs Benefits and Perks Hiring Process Life at Sandia Special Programs

Careers

[View All Jobs](#)



Turn your passion for engineering into a career.
Solve challenging national-security problems that defy easy textbook answers.

Career possibilities

- » [Aerospace Engineering](#)
- » [Bioscience](#)
- » [Business Support & Operations](#)
- » [Chemistry & Chemical Engineering](#)
- » [Computer Science](#)
- » [Cybersecurity](#)
- » [Electrical Engineering](#)
- » [Geoscience](#)
- » [Materials Science](#)
- » [Mechanical Engineering](#)
- » [Nuclear Engineering](#)
- » [Physics](#)
- » [Systems Engineering](#)

Is your career missing from the list? [View all job openings](#) instead.

Announcements

- Download our [recruiting iPad app](#) from the App Store today
- Transitioning Military: Learn about our [Wounded Warrior Career Program](#)
- Check out our [recruiting brochure](#) (PDF, 2.3 MB)

LOCATIONS

Questions?

I have no idea what you're talking about...



forums.archeagegame.com

...so here's a bunny with a pancake on its head.