

WSJ-7

Receiver Design Techniques to Maintain Sensitivity in the Presence of Large Blockers

Travis Forbes




- Blockers in Wireless Systems: Where Do They Come From?
- Circuit Level Effects of Large Blockers
 - Saturation, Nonlinearity, and Mixing
- On-Chip Blocker Mitigation Approaches
 - Harmonic Rejection Receivers
 - N Path Filters and Mixer-First Receivers
 - Self-Interference Cancellation
- Conclusion



- Cellular (4G/5G/6G)
- Wifi
- Bluetooth
- TV/Satellite
- And more...



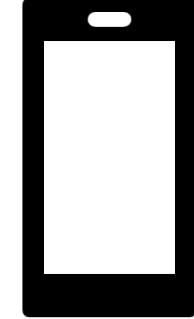
- Radars
 - Weather
 - Altimeter
 - Automotive






Many radios in a device!

Frequency Division Duplex (FDD)

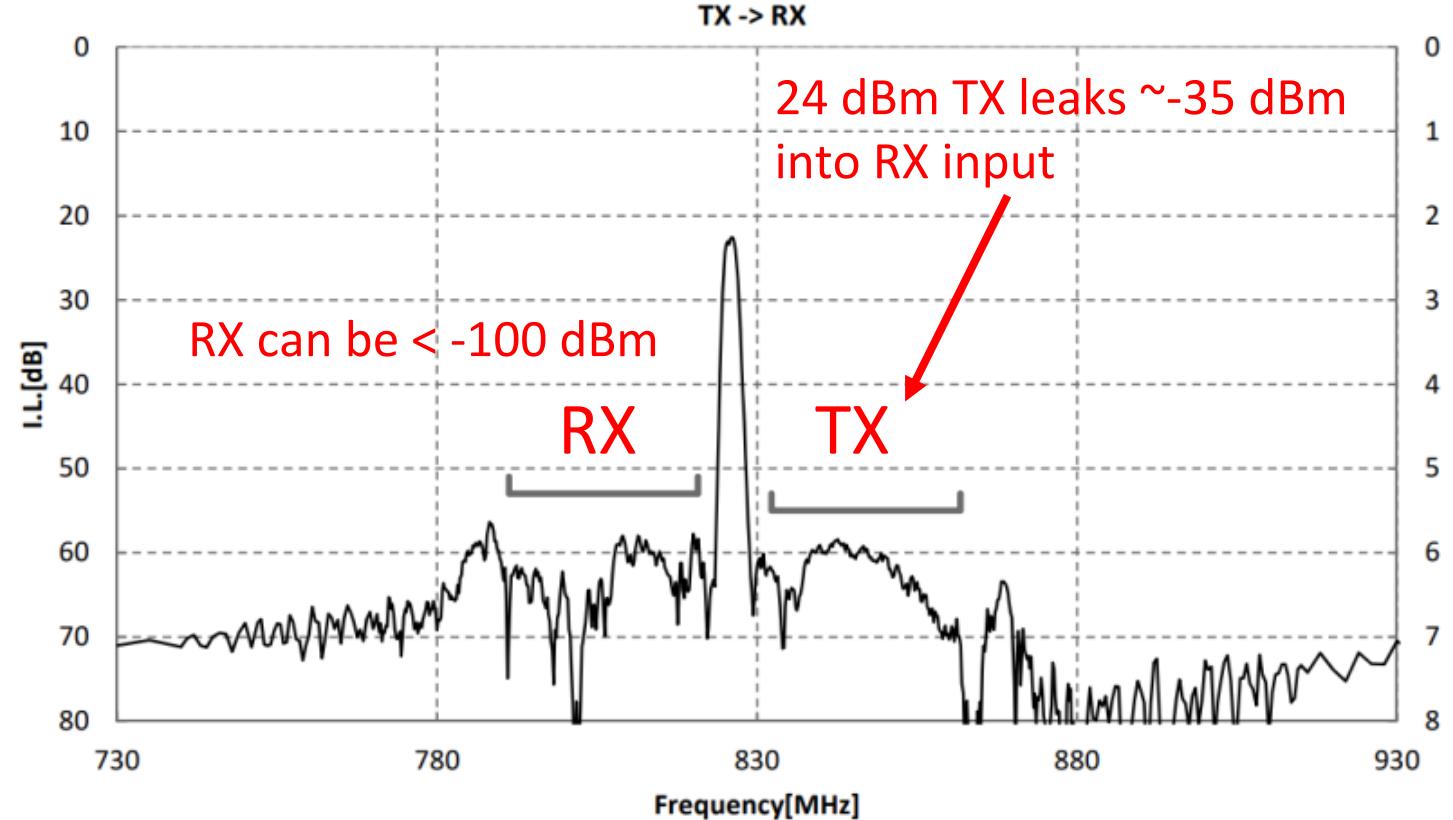


Example Murata SAYAP806MBA0C0A

Radar Systems

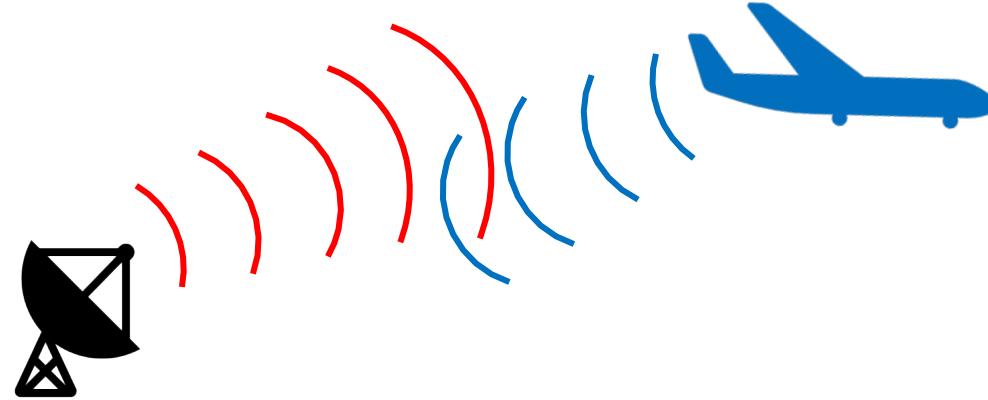

- Same frequency transmit/receive
 - TX-RX time delay in radar sets
“blind range”
 - TX-RX same time in full-duplex
- In-band blocker!


Full-Duplex Communications

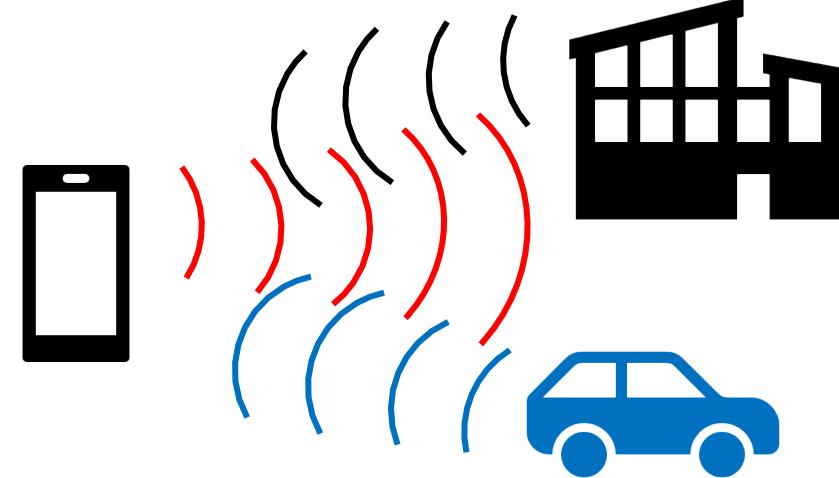


Simple Car Example

$$\begin{aligned}
 \text{[} \text{]} &= 24 \text{ [} \text{]} & \text{[} \text{]} \text{ [} \text{]} &= 1 & \text{[} \text{]} &= 3 \text{ [} \text{]} \\
 \text{[} \text{]} \text{ [} \text{]} &= 100 \text{ [} \text{]}^2 & \text{[} \text{]} \text{ [} \text{]} &= 0.35 \text{ [} \text{]} @ 850 \text{ [} \text{]}
 \end{aligned}$$

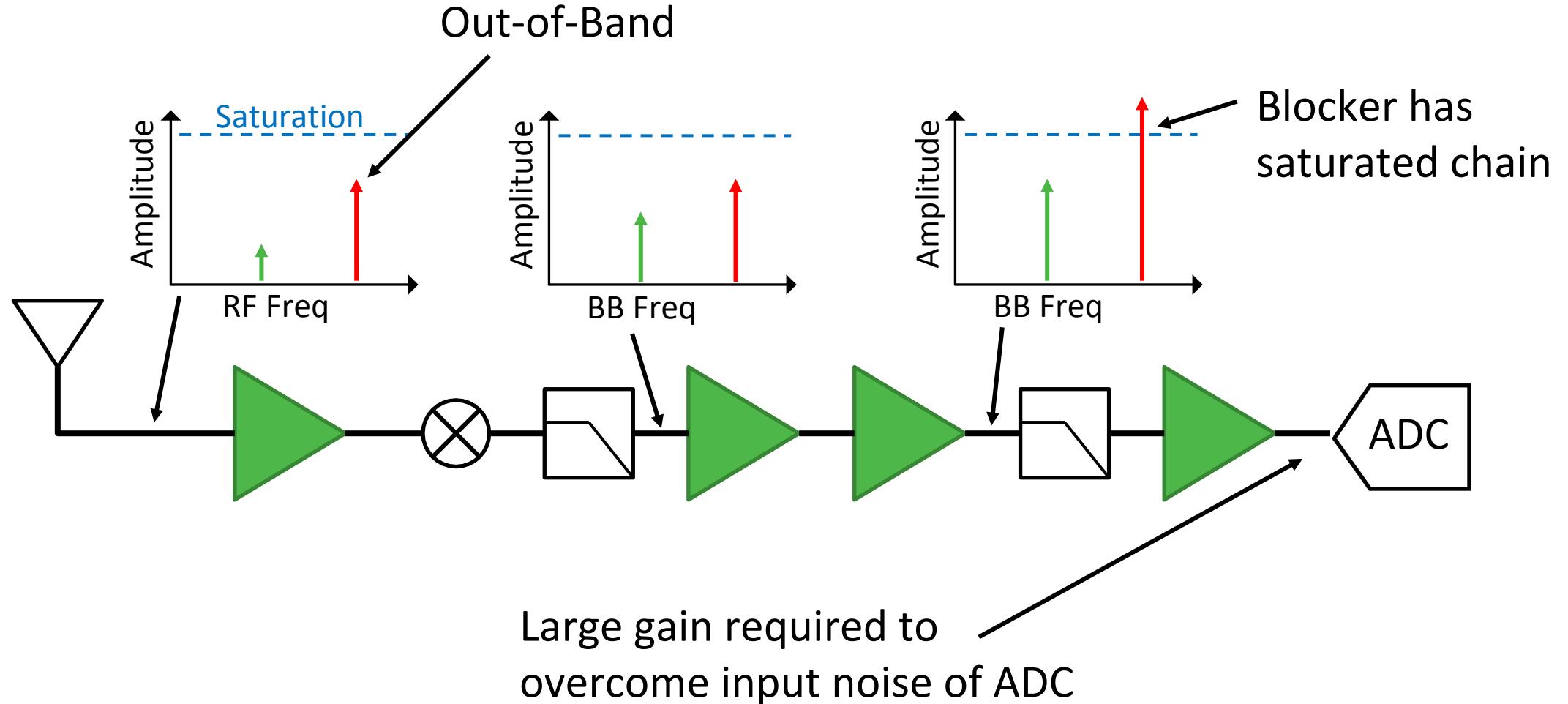
$$P_{RX} = \frac{P_{TX} G_{ANT}^2 \lambda^2 \sigma_{CAR}}{(4\pi)^3 R^4} = -17 \text{ dBm}$$



Make sure to
prevent aliasing!


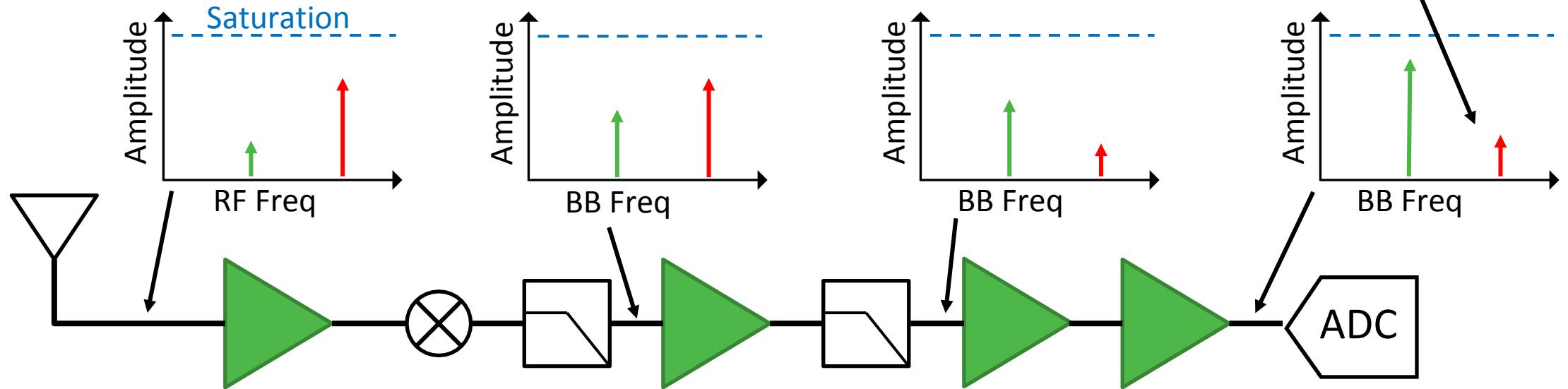


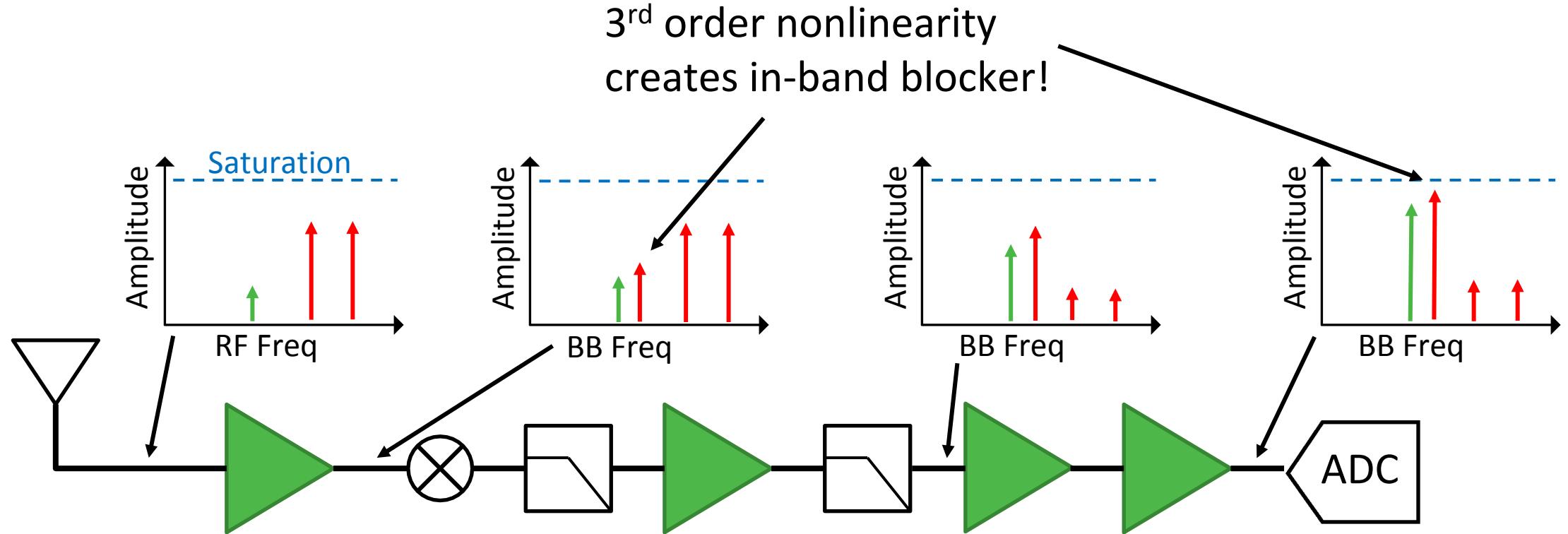Much easier to
filter at baseband
when possible




Consider 3rd order
LNA nonlinearity

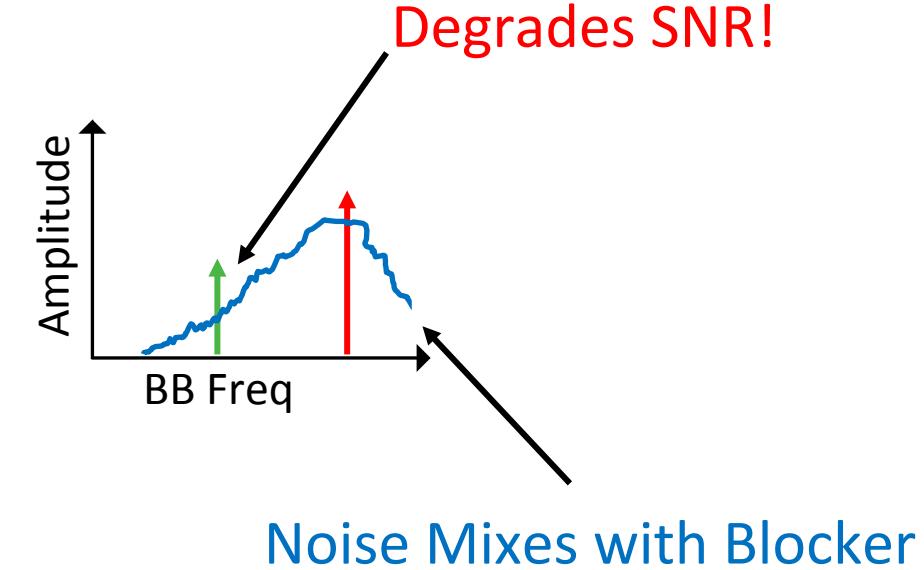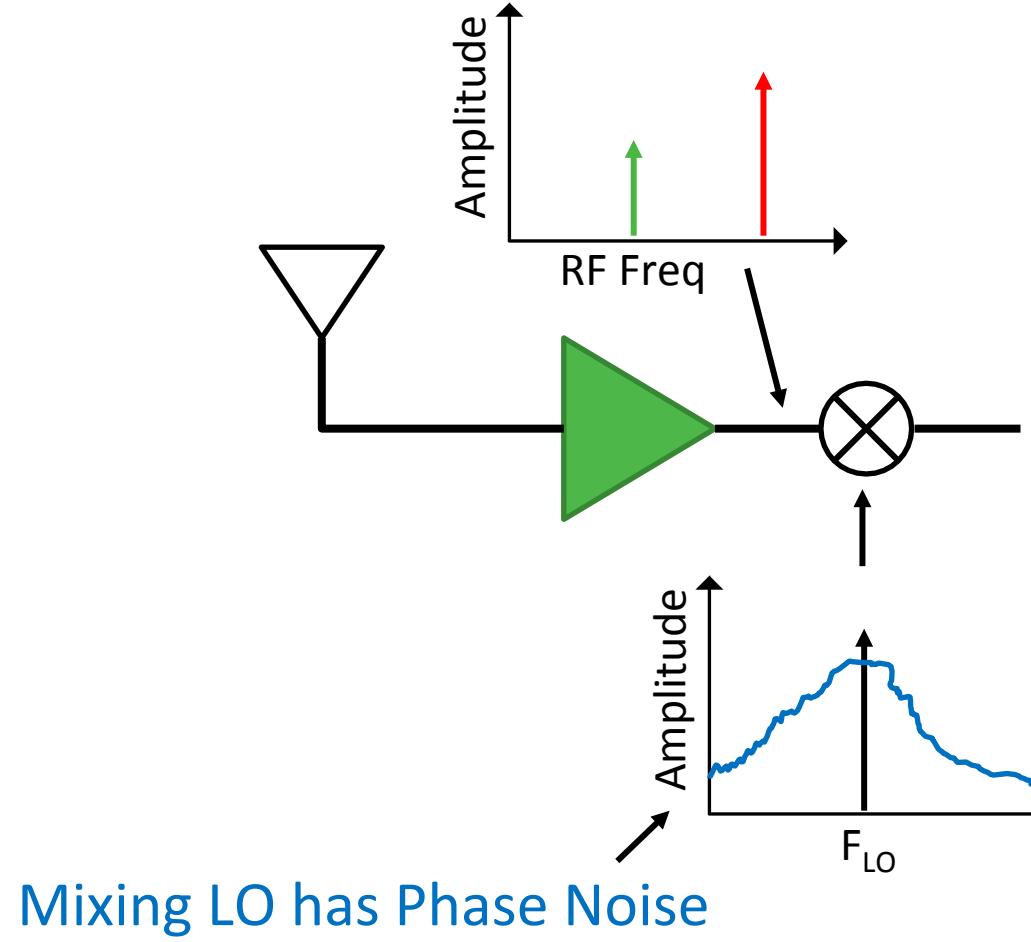3rd order nonlinearity creates tones at $2f_1 - f_2$ (shown)
and $2f_2 - f_1$




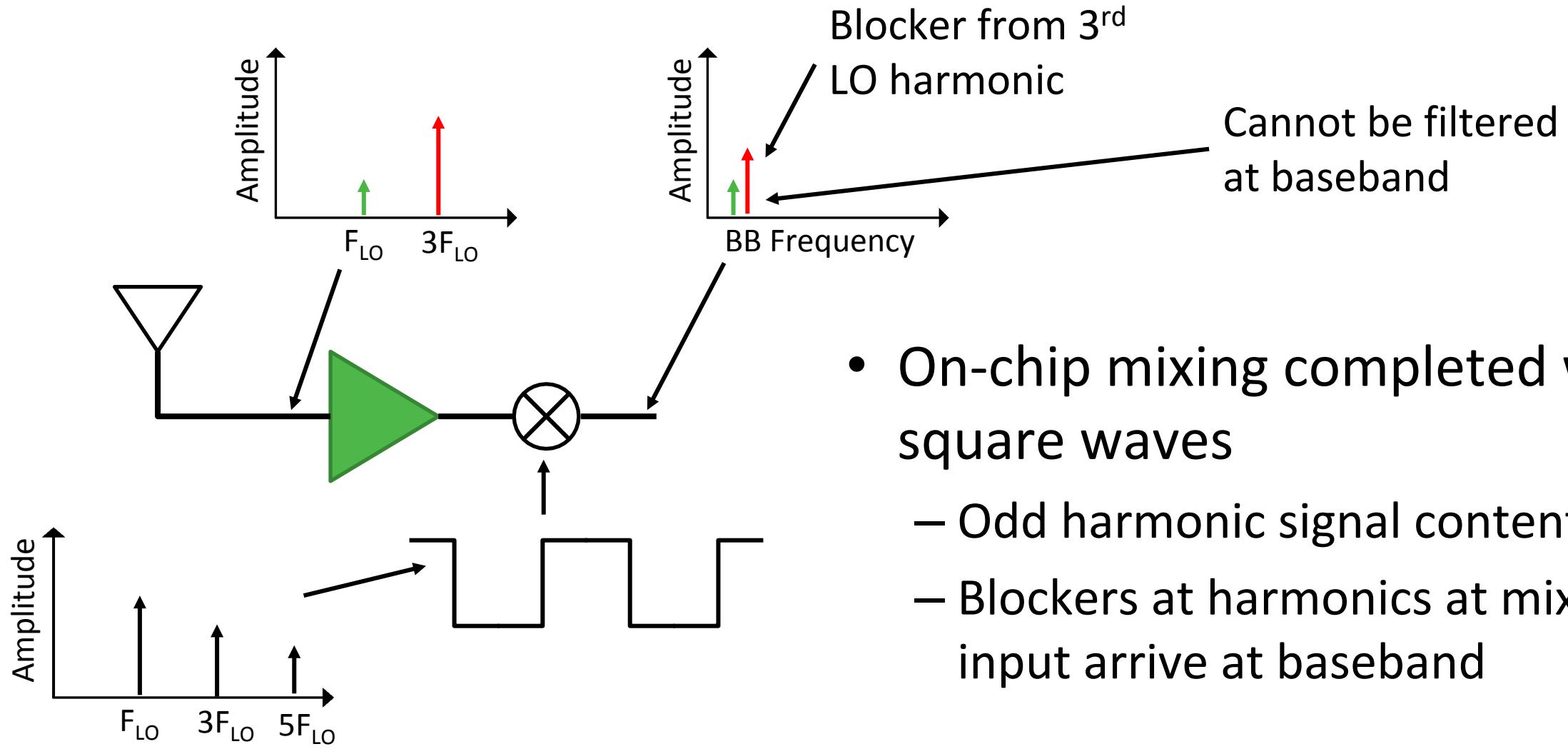- Part of a metric called blocker noise figure
 - Can also be from nonlinearity




- On-chip mixing completed with square waves
 - Odd harmonic signal content
 - Blockers at harmonics at mixer input arrive at baseband

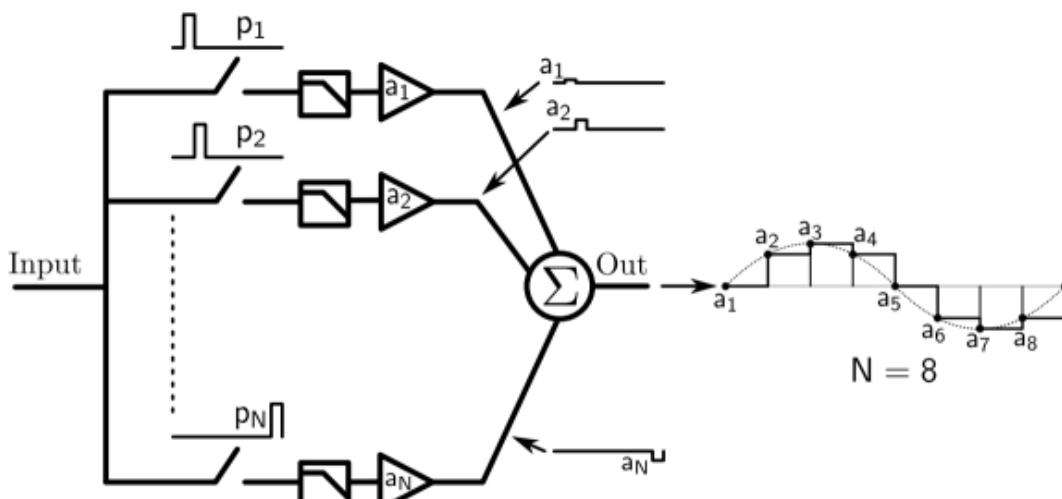
- Synthesize effective sinusoid
 - 3x 50% duty cycle paths with gains
 - $1/N$ duty cycle paths (N) with gains
 - Rejects $N-2$ harmonics



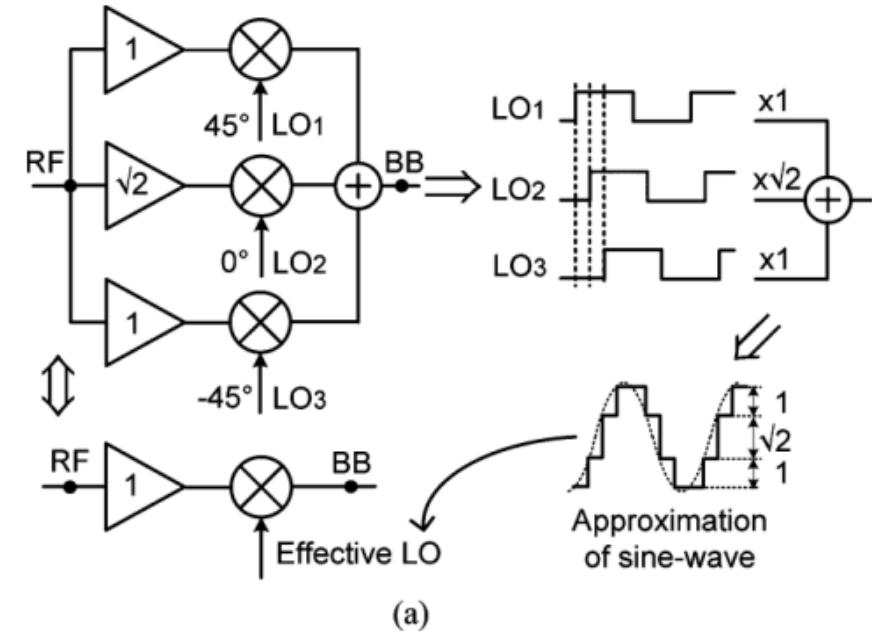
Molnar et al., CICC 2004
 Fig from Forbes et al., JSSC 2014



1st or 7th harmonic : add up


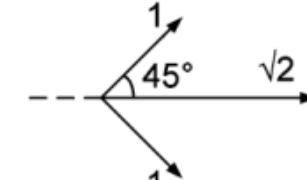


3rd or 5th harmonic : cancel

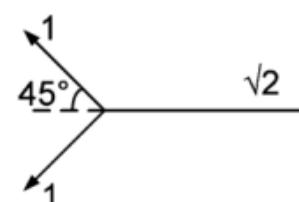

Weldon et al., JSSC 2001
 Fig from Ru et al., JSSC 2009

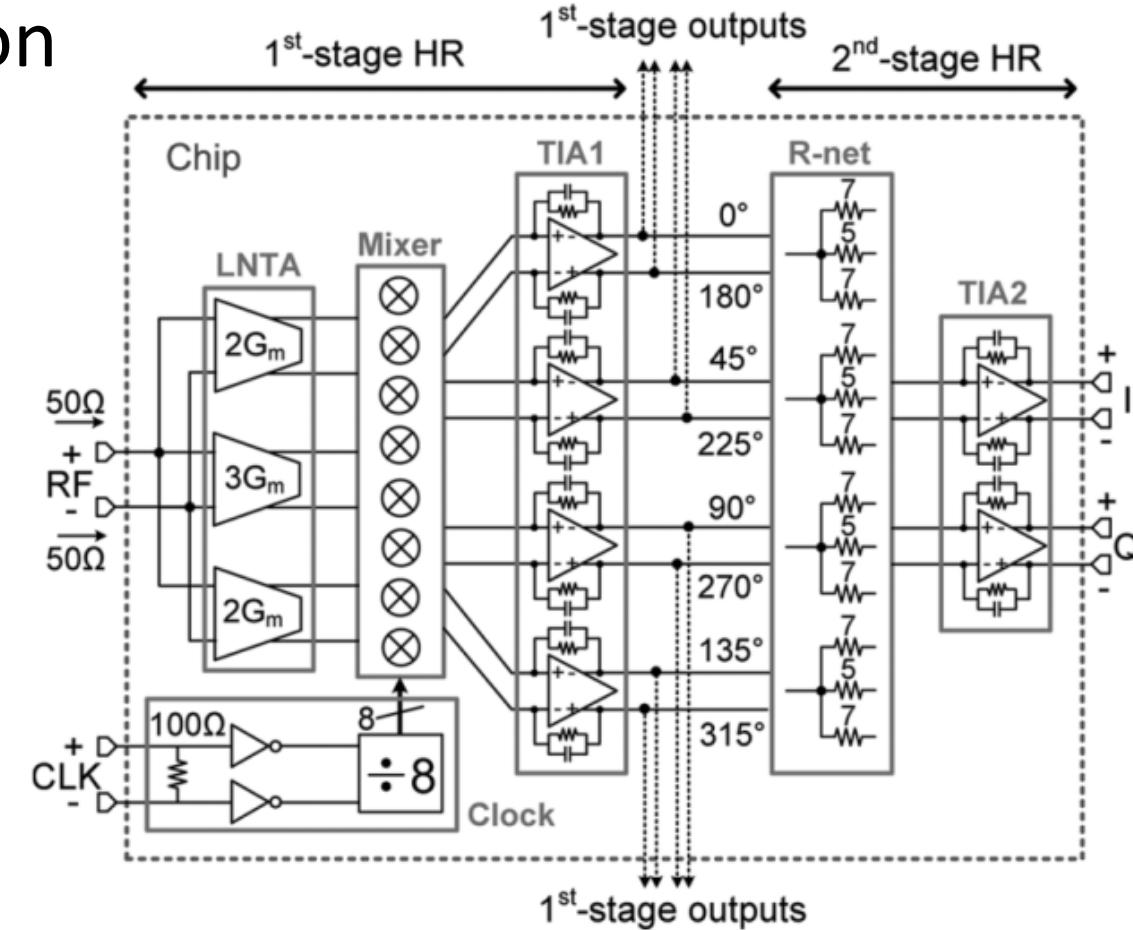
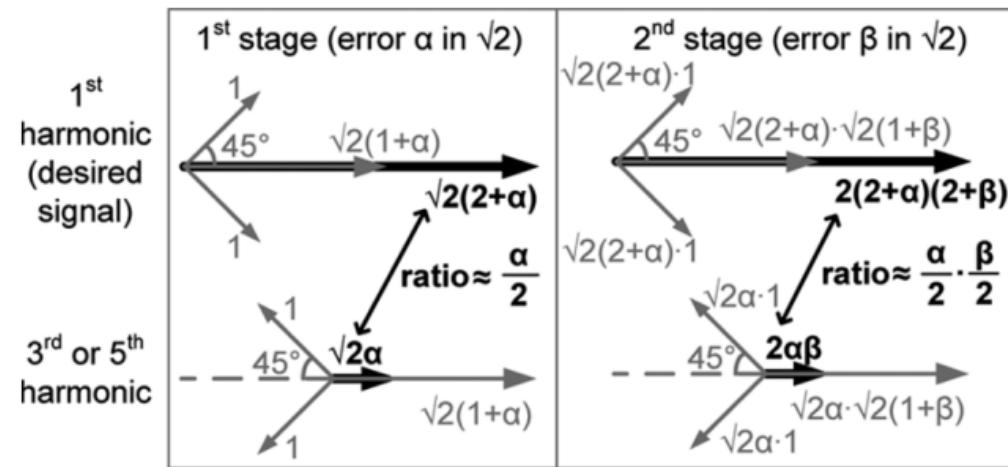
- Phase/gain mismatch limits rejection
- RF + BB gains for better rejection
 - Two gain mismatches (<1) multiply
 - Baseband two stage does not do this



Ru et al., JSSC 2009


>60 dB HR3

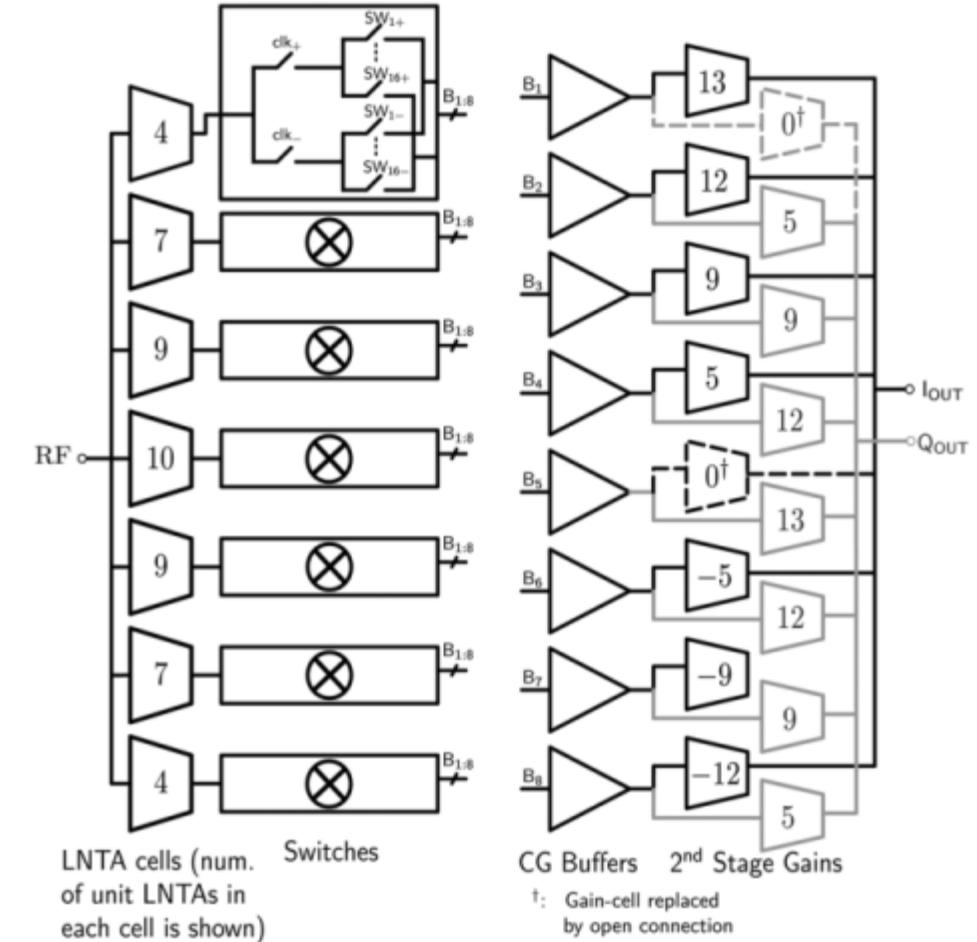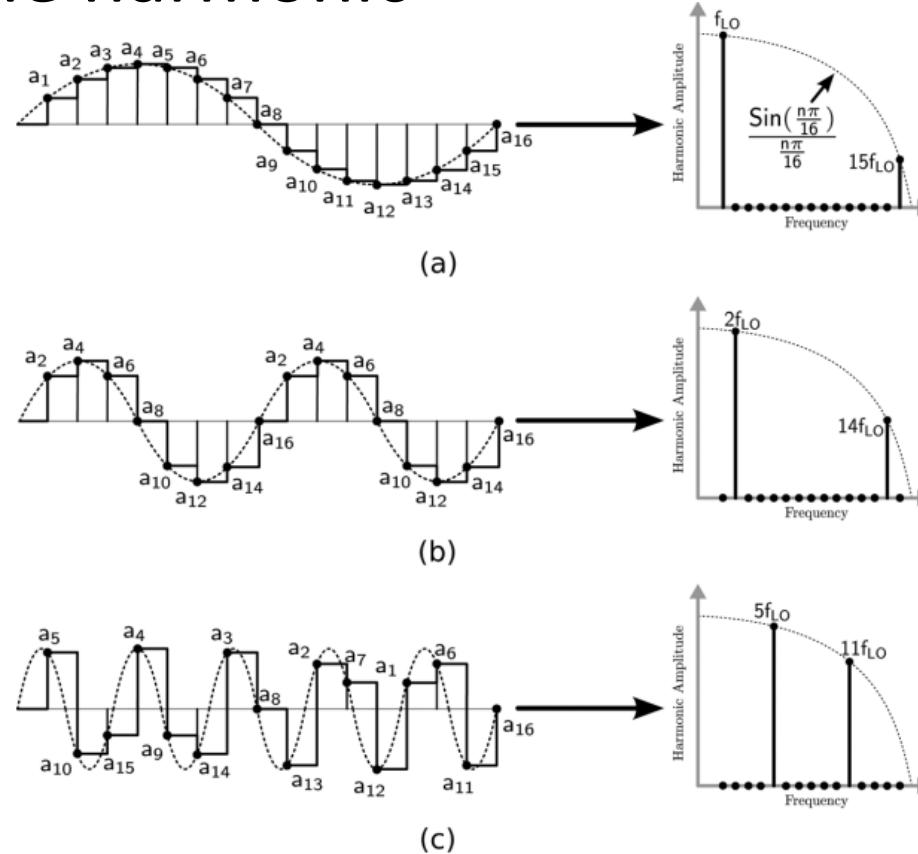- You can synthesize more than one harmonic



Forbes et al., JSSC 2013

>72 dB HR3

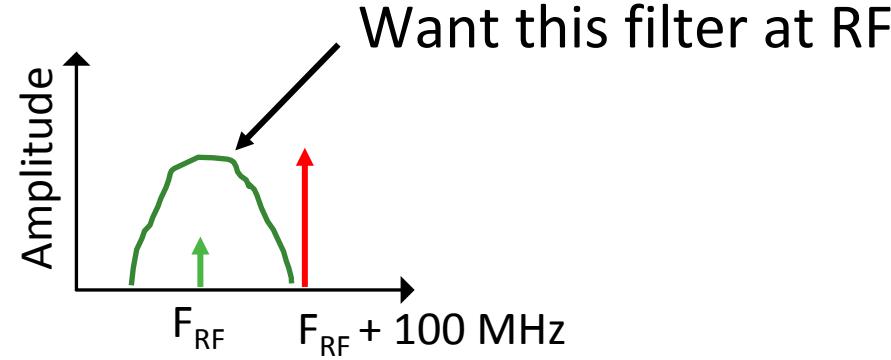


What Q for 20 MHz Filter?

Frequency (GHz)	Quality Factor
0.5	25
1	50
3	150
6	300
24	1200
60	3000
100	5000



- Desire to move with operating band
- Very high Q!
- Can we do it on-chip?
 - Typically an acoustic technology

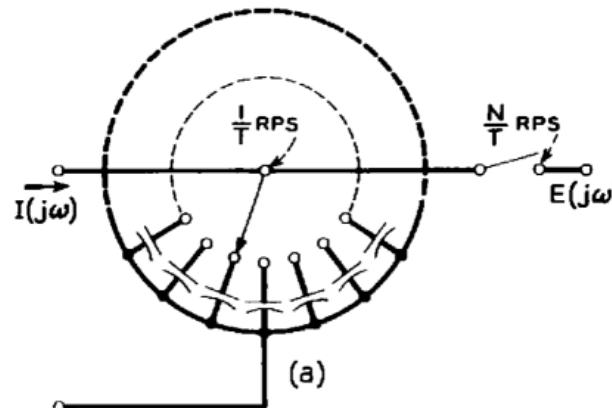- Rotate input onto N capacitors in a cyclic period
 - Creates high-Z at the clocking frequency
 - High-Q programmable filter at




Franks and Sandberg, Bell Labs 1960

- Harmonic response still a challenge

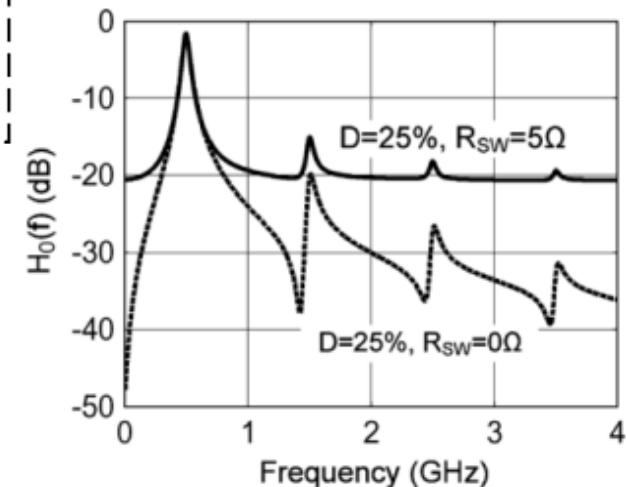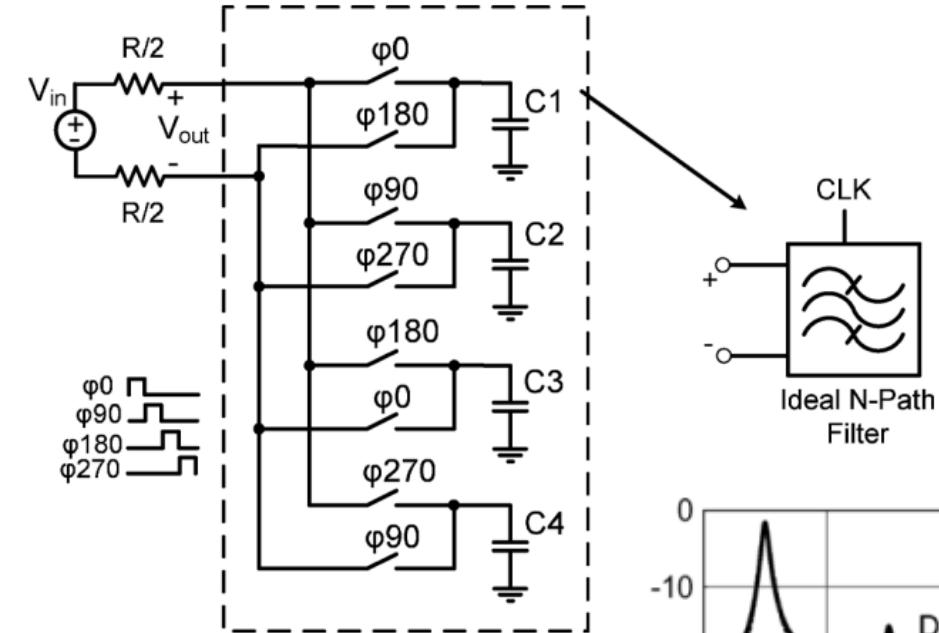


Ghaffari et al., JSSC 2011

- Bandstop filters


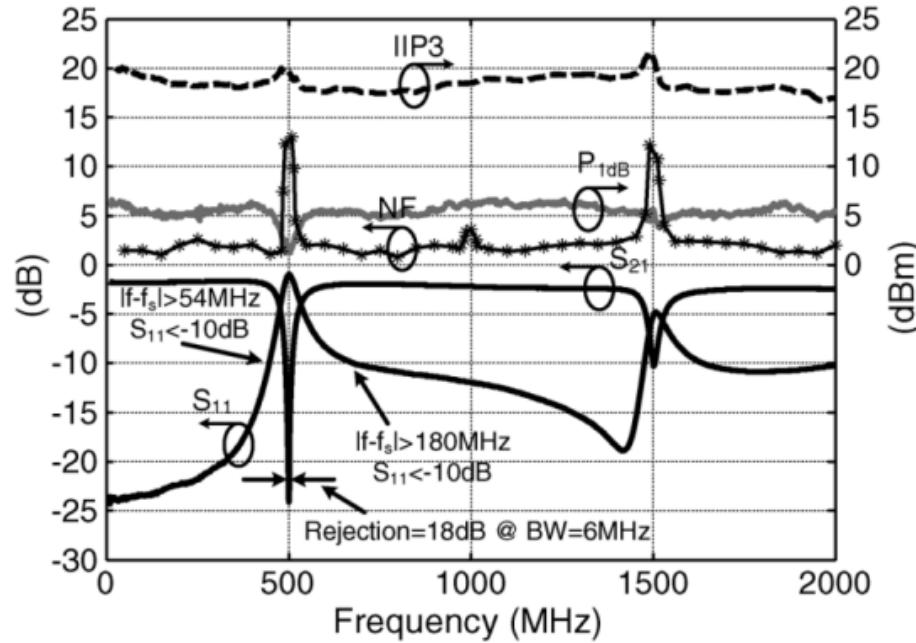


Ghaffari et al., JSSC 2013

- Passive voltage gain also possible

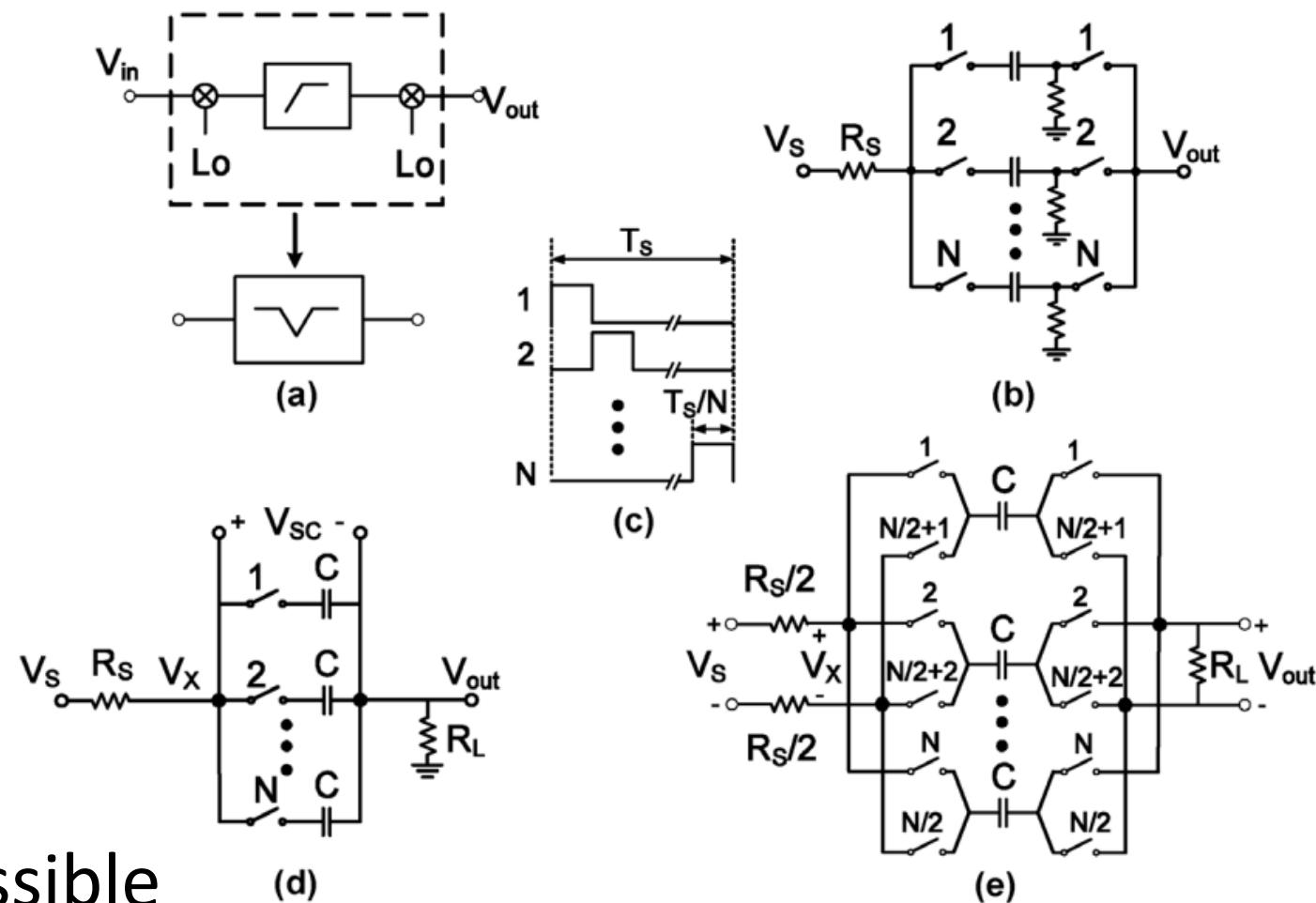


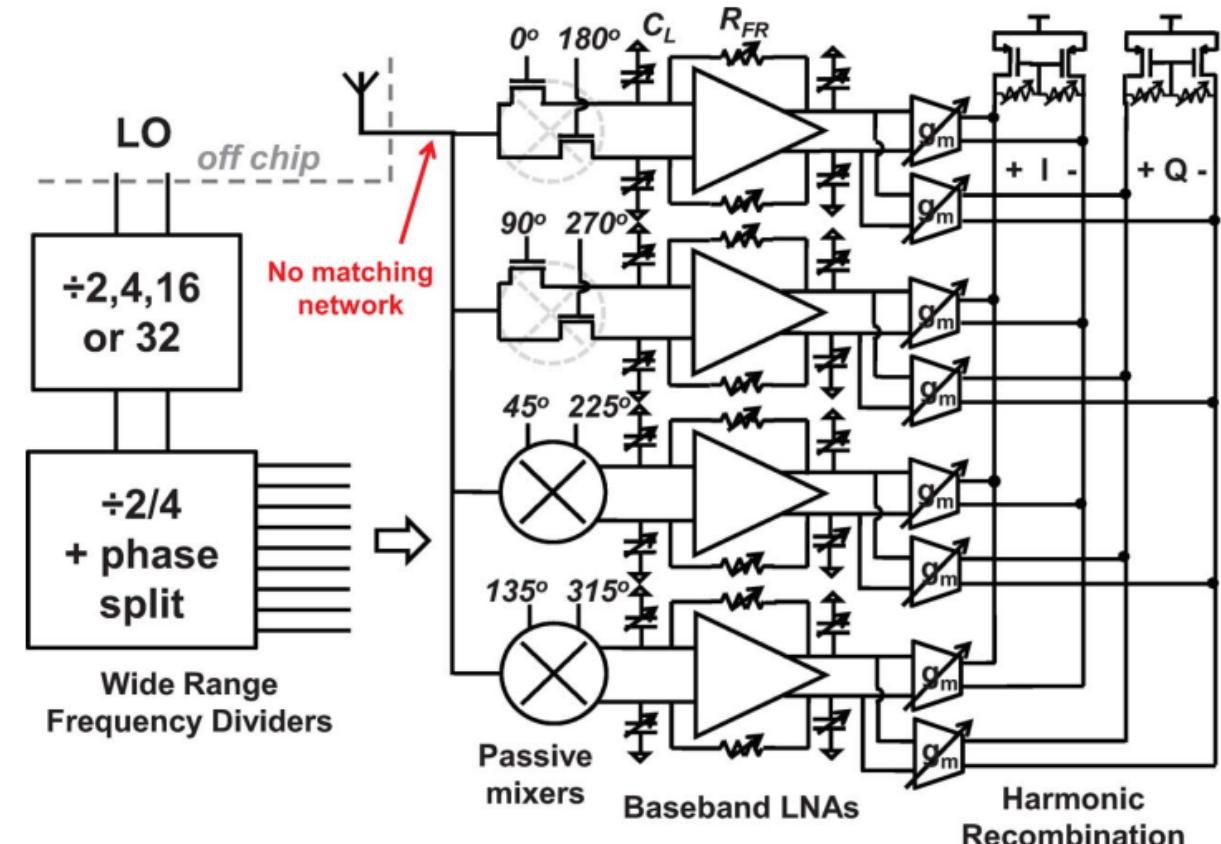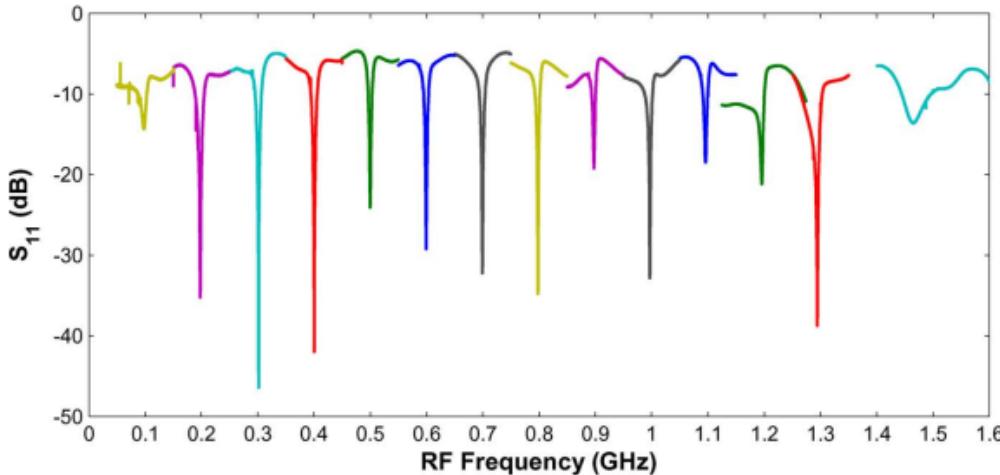- Remove the input LNA
 - High linearity
 - Match through mixer
- Can include harmonic rejection
- Lo feedthrough challenge




Andrews et al., JSSC 2010

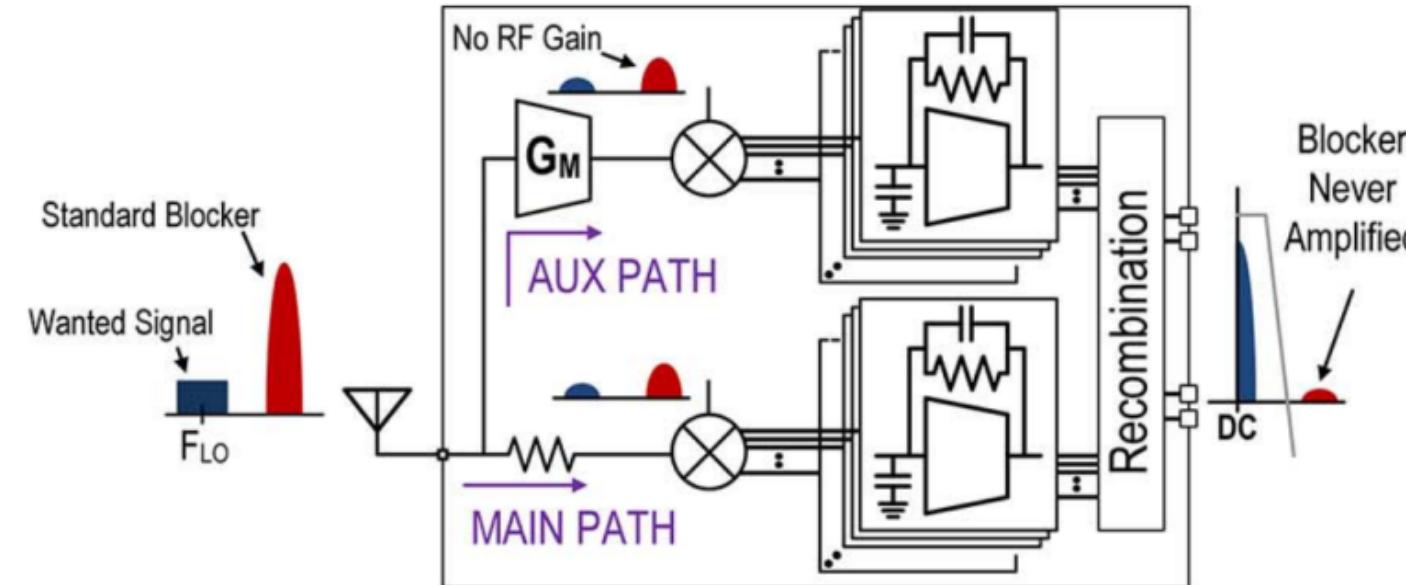- Noise cancellation possible with 2 receive paths
 - Baseband or RF



Murphy et al., JSSC 2012

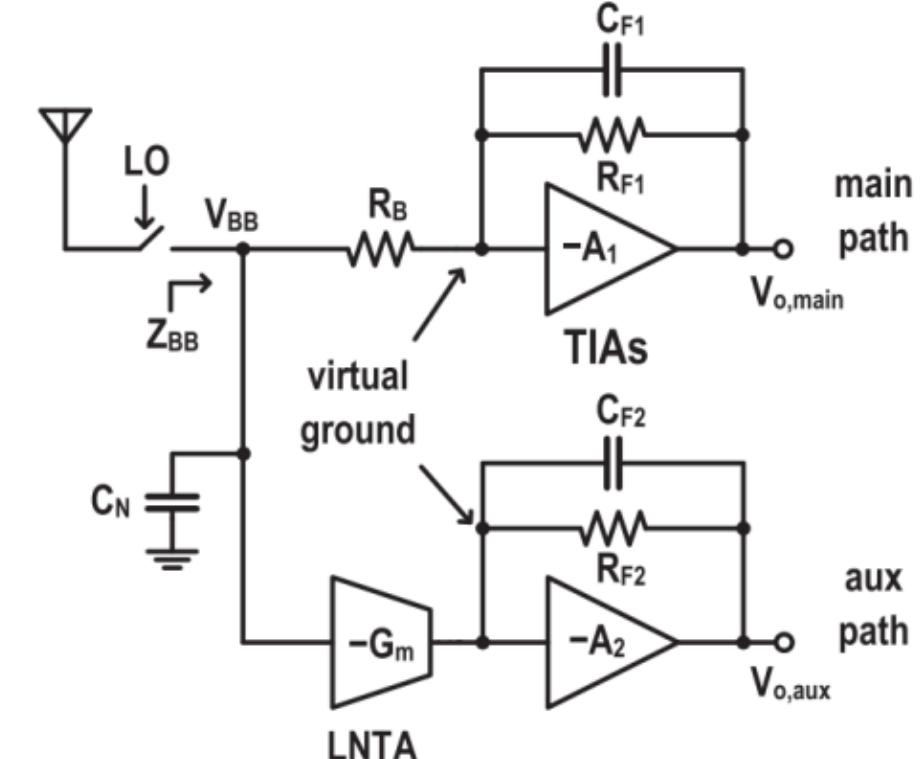


Bhat et al., JSSC 2021

	Bhat JSSC 2021	Murphy JSSC 2012	Lien JSSC 2017	Andrews JSSC 2010	Krishnamurthy JSSC 2020
Architecture	MF BB NC	MF RF NC	MF Cap Fdbk	Mixer-First	MF 40 dB/dec
NF (dB)	2.5-5	1.9	2.3-5.4	3-5	4.3-7.6
Frequency (GHz)	1-6	0.3-2.9	0.2-8	0.1-2.4	0.2-2
Gain (dB)	22	72	21	40-70	13
OIP3 (dBm)	18	13.5	39	25	33.3
Power (mW)	172	35-78	56-290	37-70	147-179
Process Node	22 FDX	40 nm	45 nm SOI	65 nm	28 nm

Significant out-of-band linearity!



Reasonable noise figure

Large bandwidth of operation

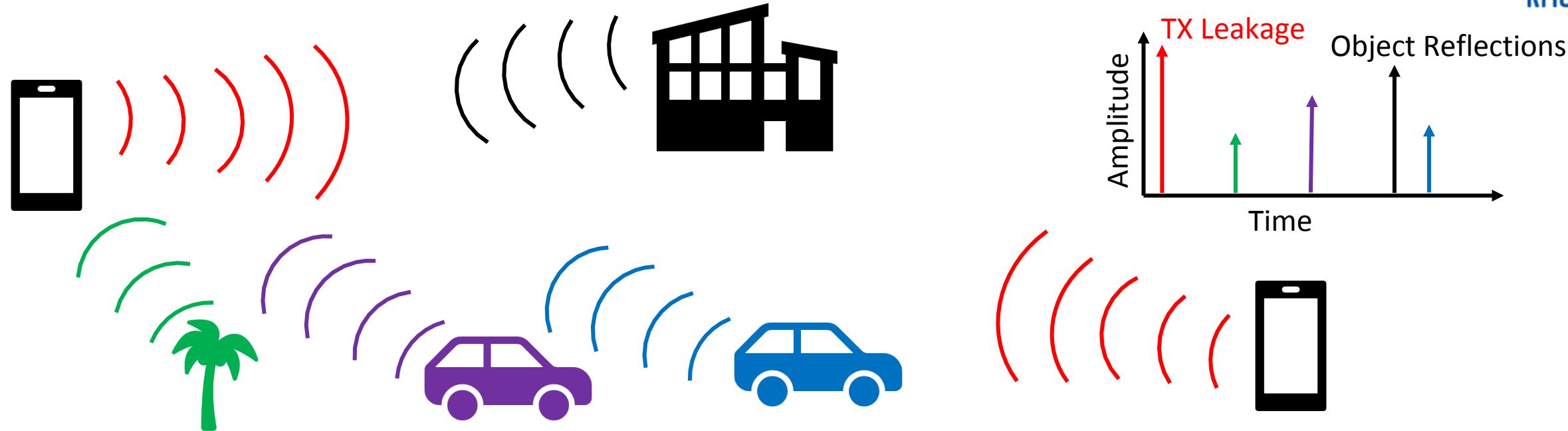


- Transmit and receive at the same frequency and time
 - Increase in spectral efficiency
- BUT you are your own worst blocker
 - In addition to traditional blockers

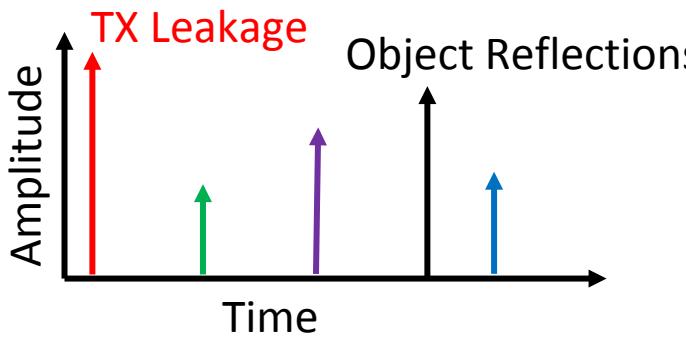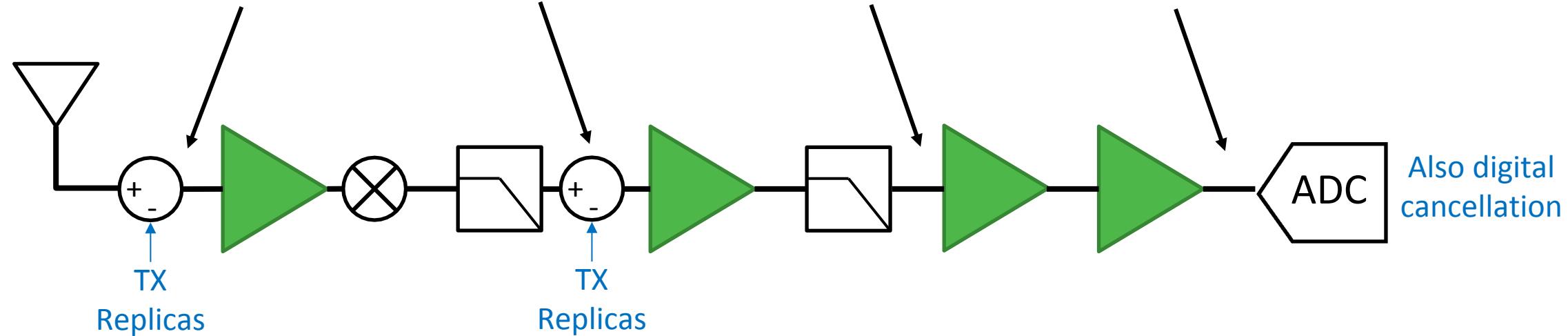Must prevent saturation and nonlinear effects throughout the receiver



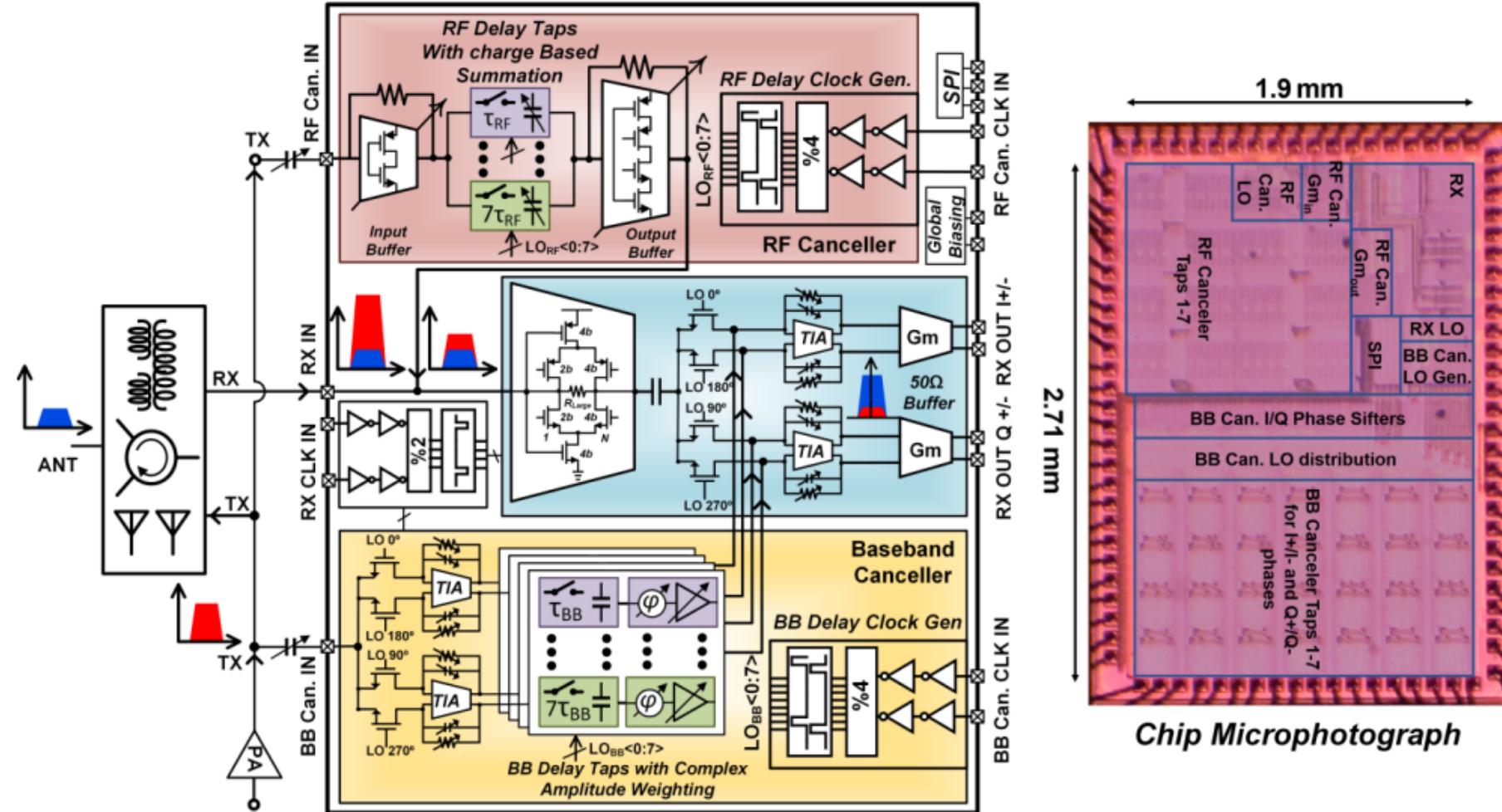- TX replica for cancellation must include all leakage and reflections
 - Delay and amplitude must be matched
 - Objects in environment major challenge



Nagaulu et al., JSSC 2021

- Blockers are present from other wireless devices and from contributions within a device
- Place filters in receive chain carefully to prevent saturation
- Mixer techniques can prevent harmonic downconversion
- N path filters and mixer first receivers enable high-Q filtering
 - Filtering follows mixing frequency
- Many research challenges to solve to make full-duplex a reality