



Marx Source

Ivan Aponte


This work was done by Mission Support and Test Services, LLC, under Contract No. DE-NA0003624 with the U.S. Department of Energy and the National Nuclear Security Administration. DOE/NV/03624--1829.



Why a Marx?


- Need a permanent pulsed power source to use for diagnostic experiments
- Most of the parts are readily available
 - Ceramic capacitors, spark gaps, power supply, coaxial cable, etc.
- Easy to design and test
 - Important considering time constraints

System Overview

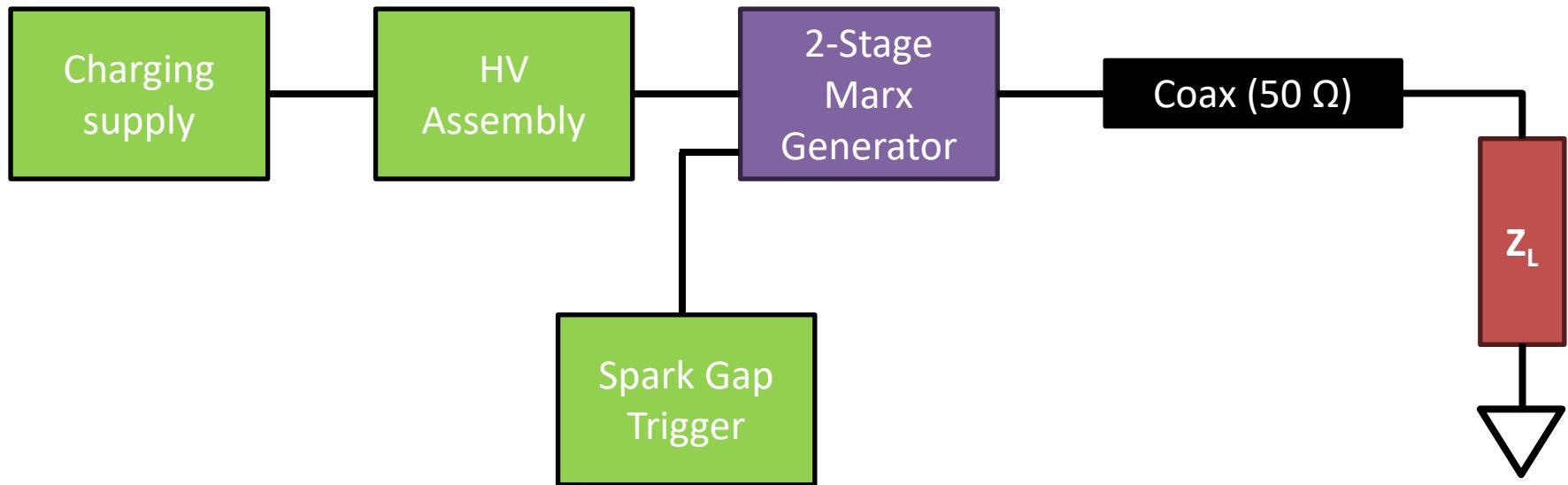

- Charging supply: Glassman HV supply (12.5 kV charge voltage, 2 mA)
- HV assembly: charging resistor & diode stack (for supply protection)
- 2 stage resistively charge Marx generator
- Coax: RG-217 or RG-8
- Load also interchangeable

Charging & High Voltage Assembly

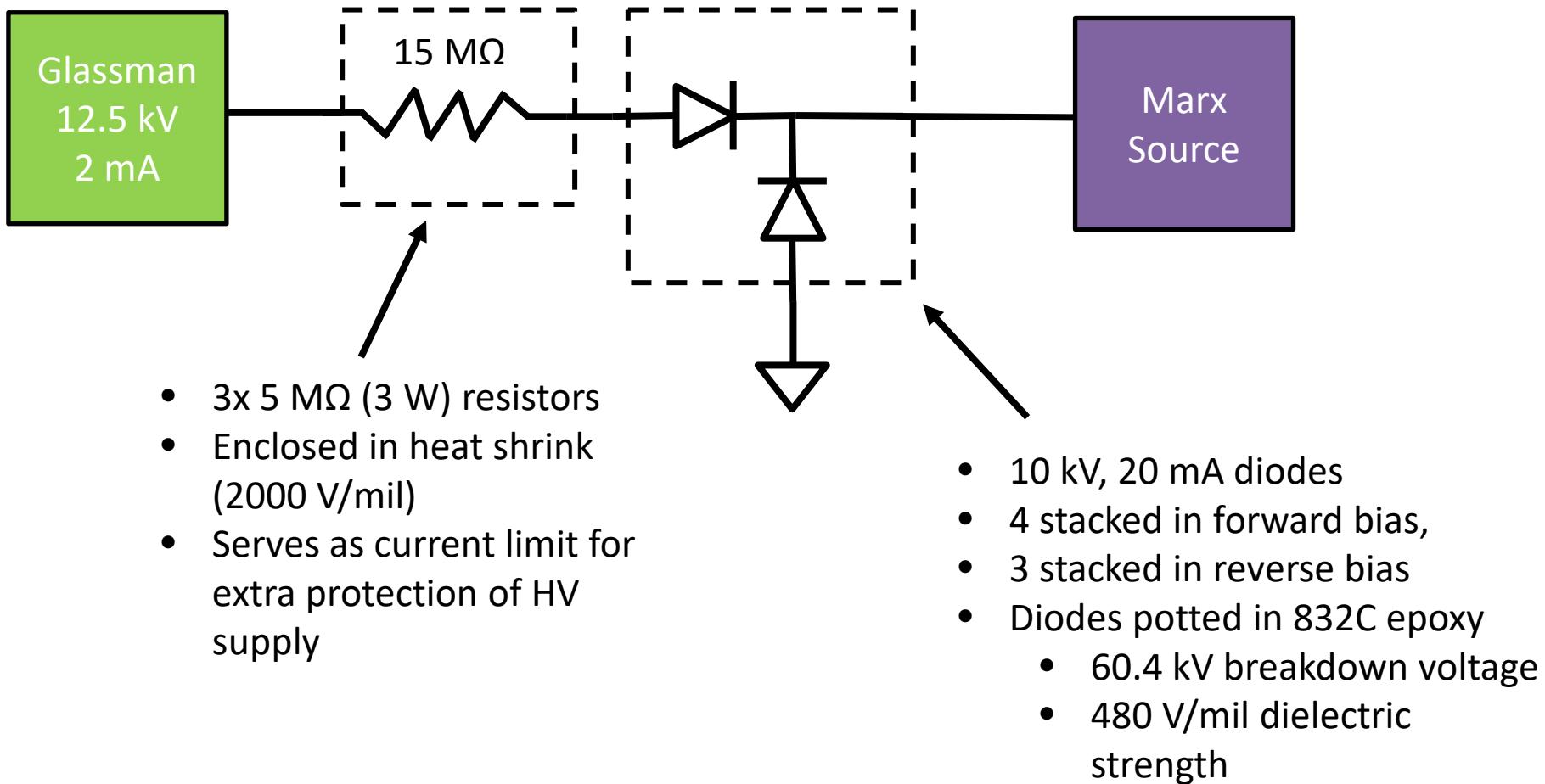

Marx Circuit


Each stage uses 3, 2 nF door knob capacitors (40 kV rated)

$$W_{marx} := \frac{1}{2} \cdot N_{stage} \cdot C_{total} \cdot V_c^2 = 0.469 \text{ J}$$

Charging time:


$$t_c := 2 \cdot R_c \cdot C_{total} \cdot N_{stage}^2 = 360 \text{ ms}$$

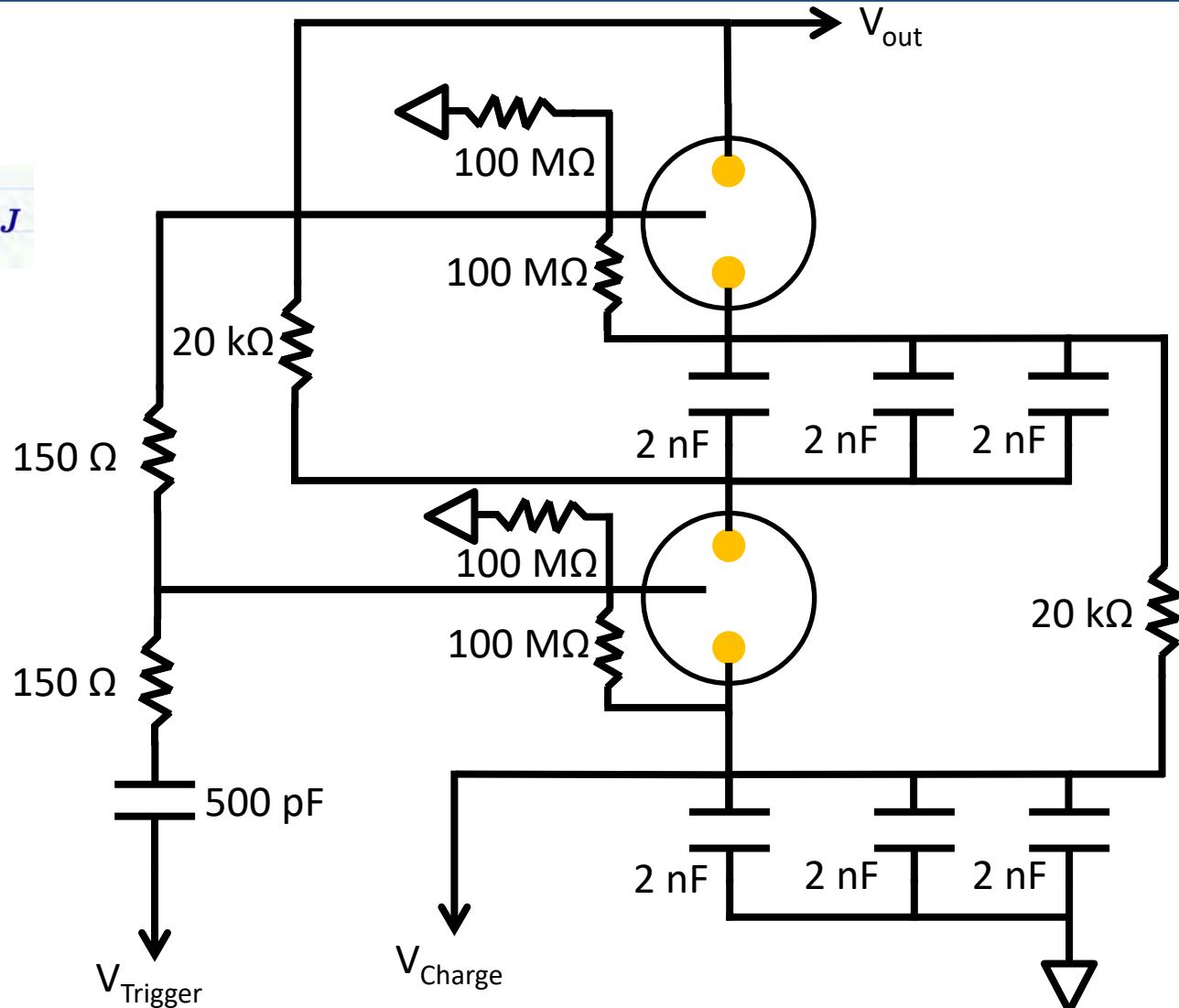- Output of Marx ~ 25 kV peak
- Midplane field distortion spark gaps as switches
- Triggered using -17.5 kV pulse




Charge and Discharge Circuits

Charge Circuit

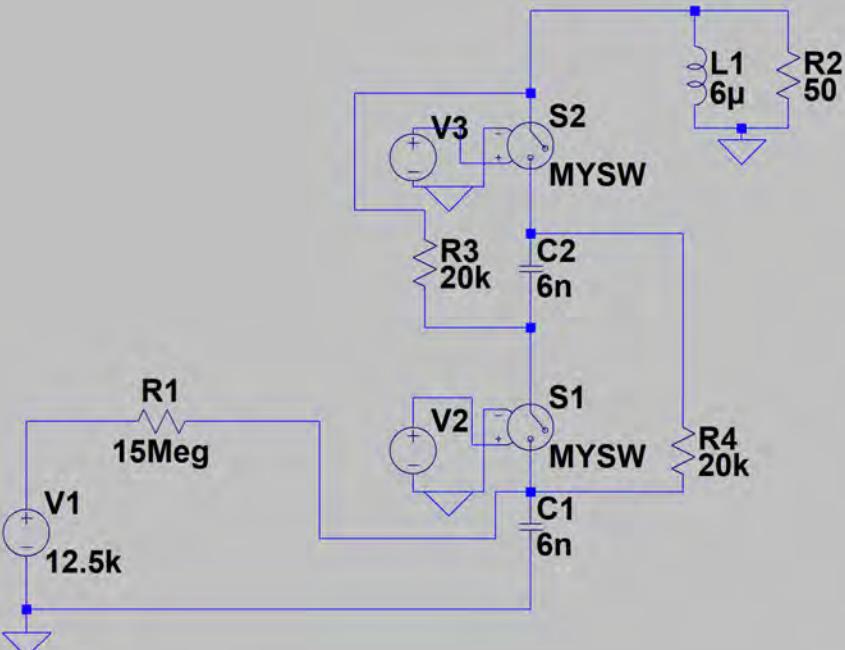


```
.model MYSW SW(Ron=10m Roff=1000Meg Vt=.5 Vh=-.4)
.tran 0 1s 10u startup
```

Discharge Circuit

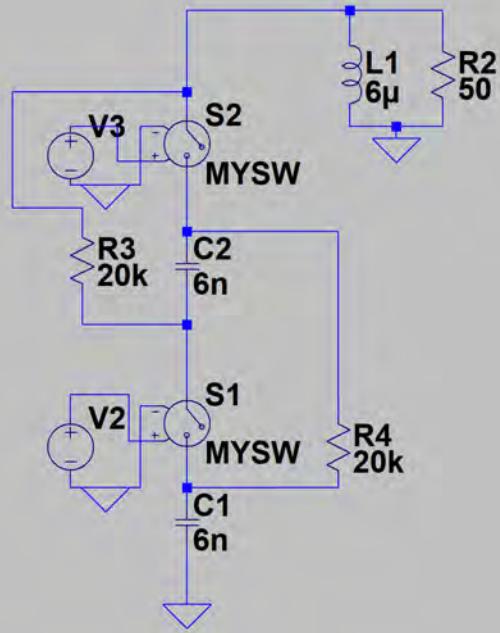


```
.model MYSW SW(Ron=10m Roff=1000Meg Vt=.5 Vh=-.4)
.tran 0 5u 0 1n
```

Charging Circuit Waveforms

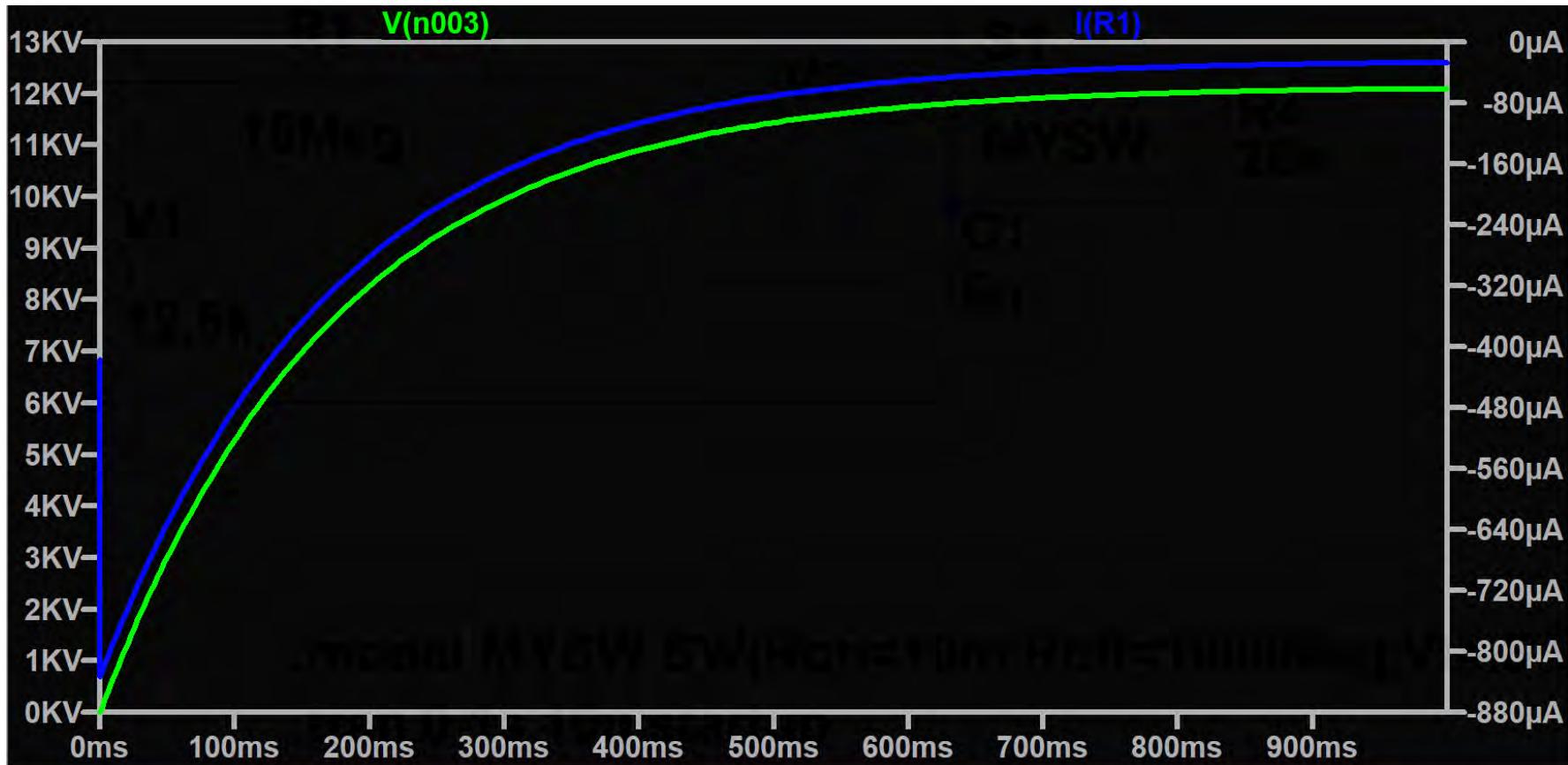


- Charge voltage – green trace
- Charging resistor current draw – blue trace
- Complete charging ~1 second, current draw peak 880 μ A, within Glassman current limit

Discharging Circuit

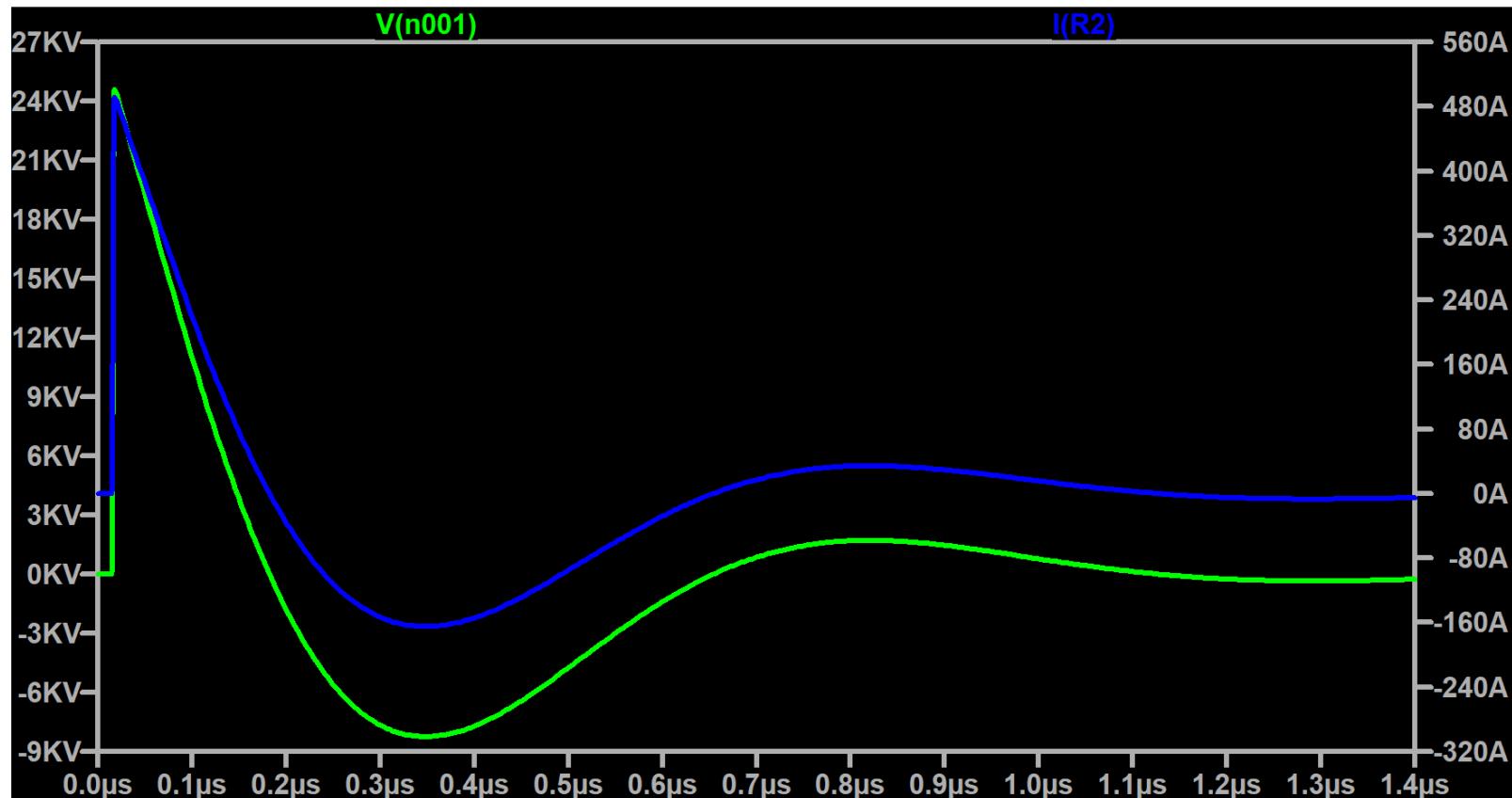


- Load voltage – green trace
- Load current – blue trace
- 24 kV peak voltage (~ 77 ns pulse width), 480 A peak current.
- Voltage and current backswing: 33.8%

Marx Rendering

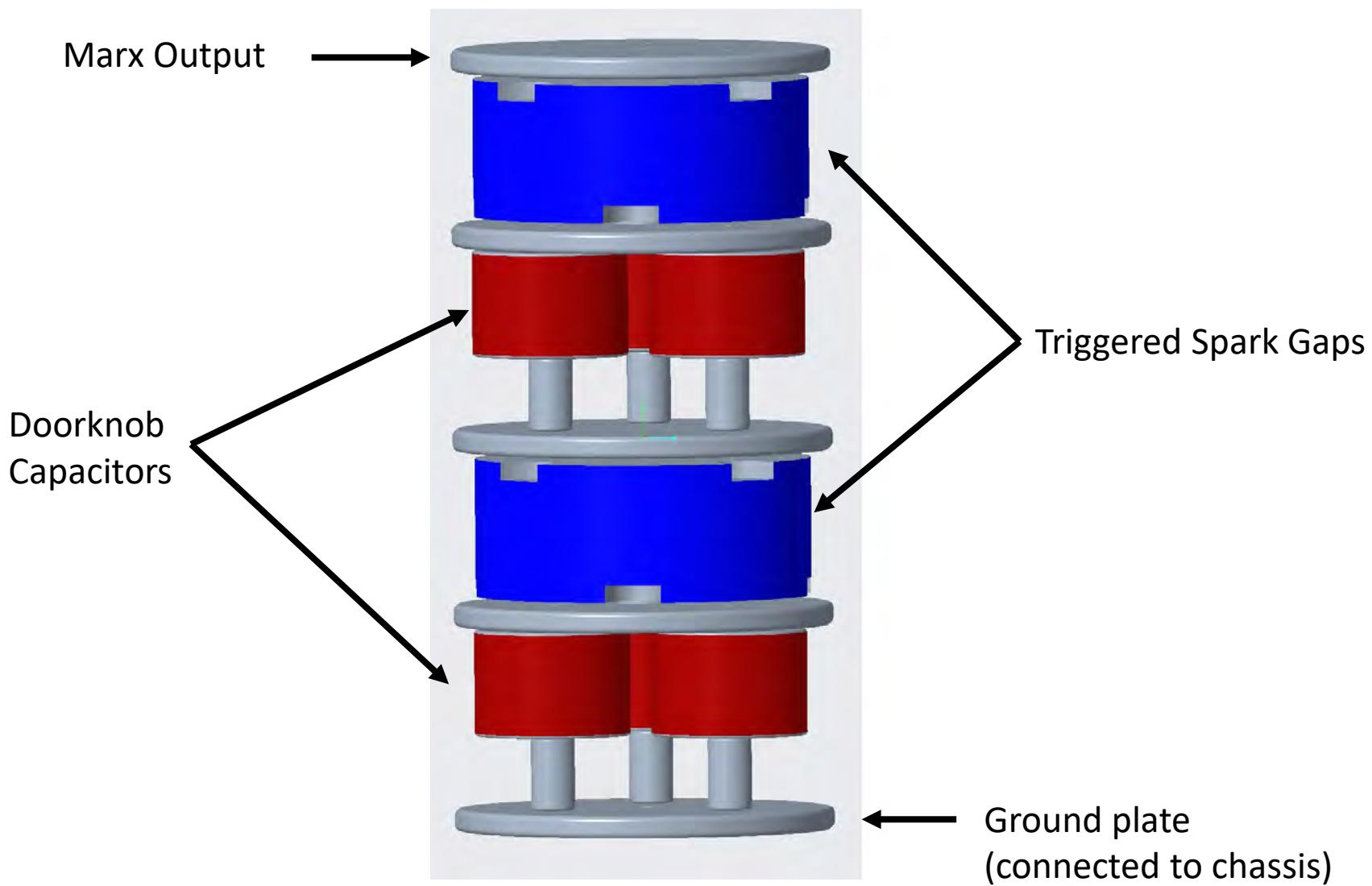


Spark Gap Trigger Overview

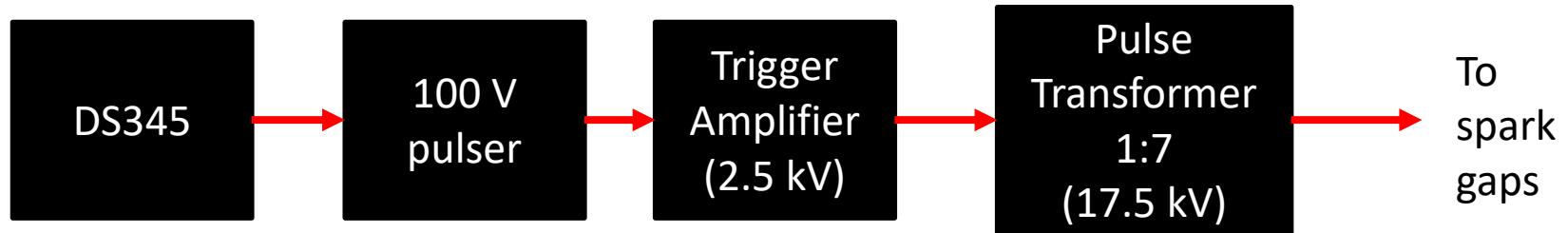

Many components are involved, but readily available!

Cable Assembly (Cross-section)

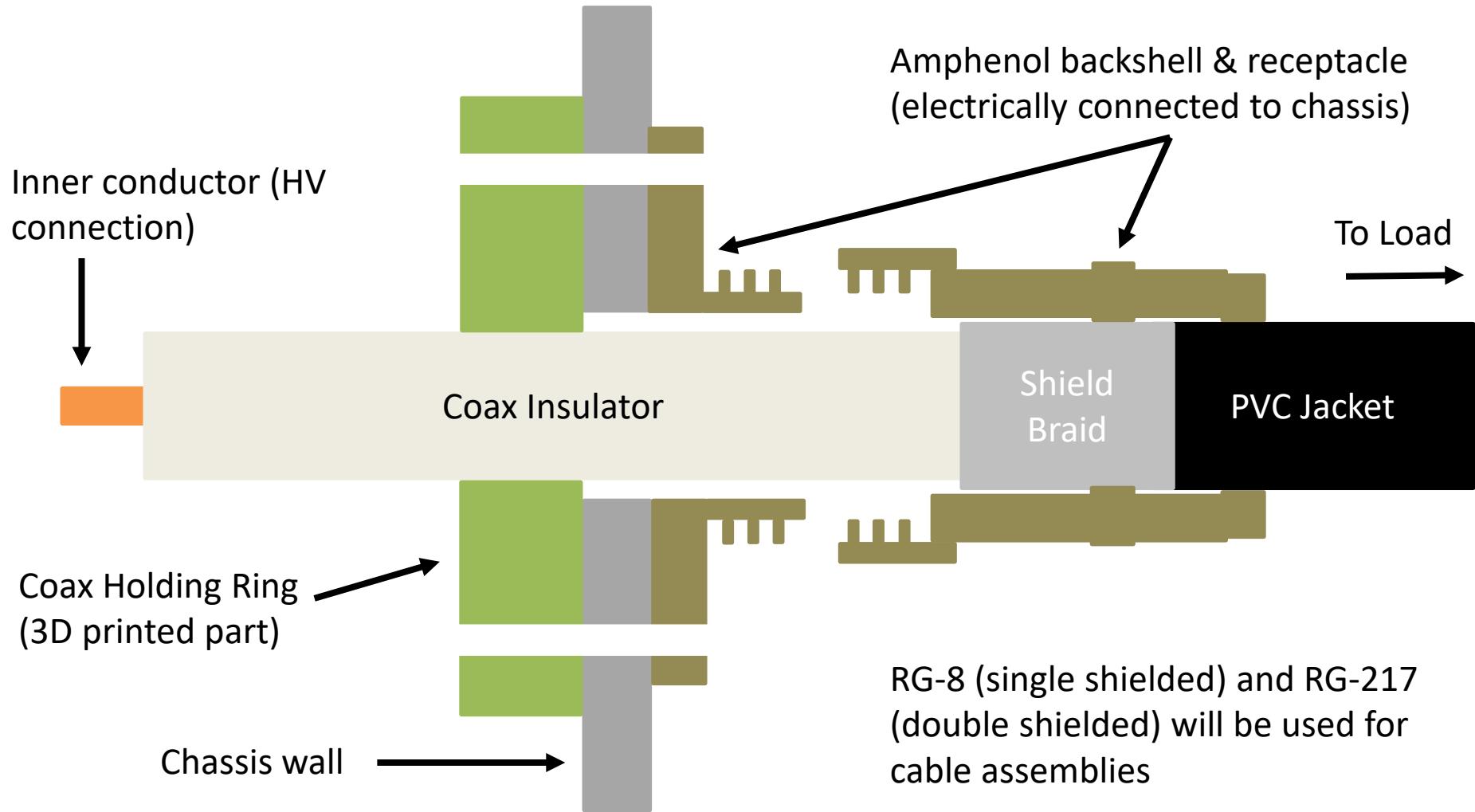

Summary & Future Work

- Parts ordered for Marx source
- Trigger circuit needs to be tested once parts arrive
- Currently setting up experiment with prototype diagnostic and different pulser
- Qualifier exam scheduled for December 11th